



## الکترونیک ۲

### فصل ۸ – تقویت کننده عملیاتی (آپ امپ)

Mohammad Ali Mansouri- Birjandi

Majid Ghadrdan

Faculty of Electrical and Computer Engineering  
University of Sistan and Baluchestan (USB)

[mansouri@ece.usb.ac.ir](mailto:mansouri@ece.usb.ac.ir) ,  
[mamansouri@yahoo.com](mailto:mamansouri@yahoo.com)



# Chapter 8 Operational Amplifier as A Black Box

دانشگاه اسلامی  
دانشگاه اسلامی  
دانشگاه اسلامی

- 8.1 General Considerations
- 8.2 Op-Amp-Based Circuits
- 8.3 Nonlinear Functions
- 8.4 Op-Amp Nonidealities
- 8.5 Design Examples



# Chapter Outline

## General Concepts

- Op Amp Properties

## Linear Op Amp Circuits

- Noninverting Amplifier
- Inverting Amplifier
- Integrator and Differentiator
- Voltage Added

## Nonlinear Op Amp Circuits




- Precision Rectifier
- Logarithmic Amplifier
- Square Root Circuit

## Op Amp Nonidealities

- DC Offsets
- Input Bias Currents
- Speed Limitations
- Finite Input and Output Impedances



# Basic Op Amp



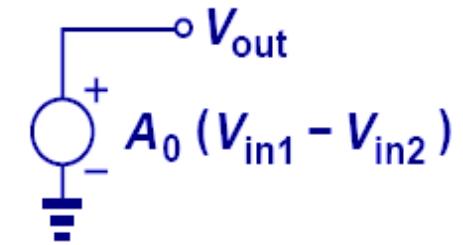
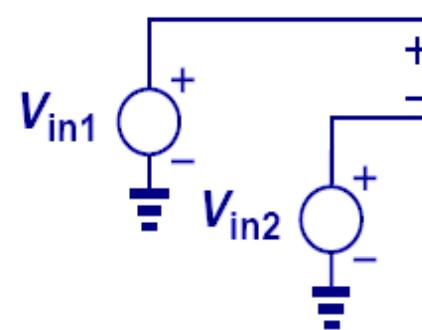
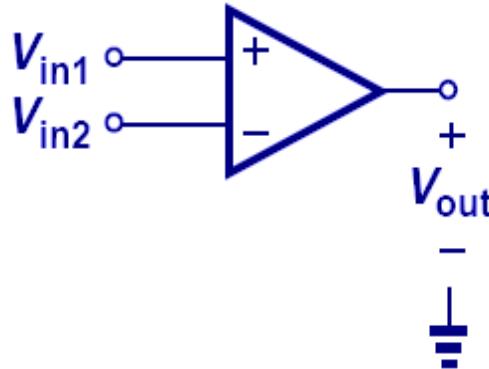


$$V_{out} = A_0(V_{in1} - V_{in2})$$

- Op amp is a circuit that has two inputs and one output.
- It amplifies the difference between the two inputs.



# Inverting and Non-inverting Op Amp

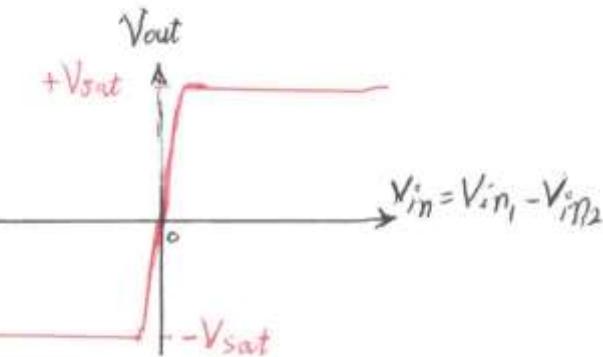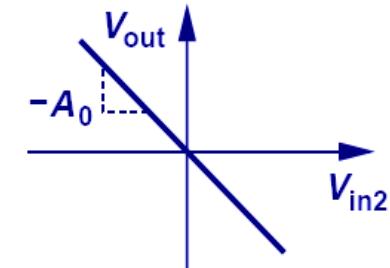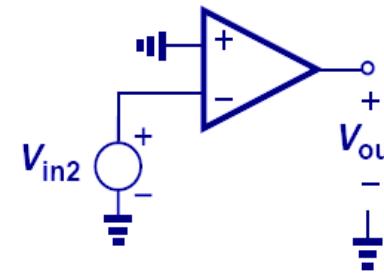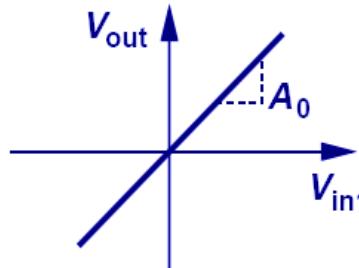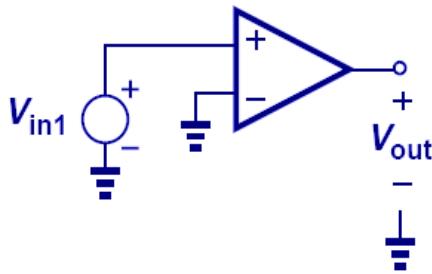


- If the negative input is grounded, the gain is positive.
- If the positive input is grounded, the gain is negative.



# Ideal Op Amp


- **Infinite gain**
- **Infinite input impedance**
- **Zero output impedance**
- **Infinite speed**

# Ideal Op Amp

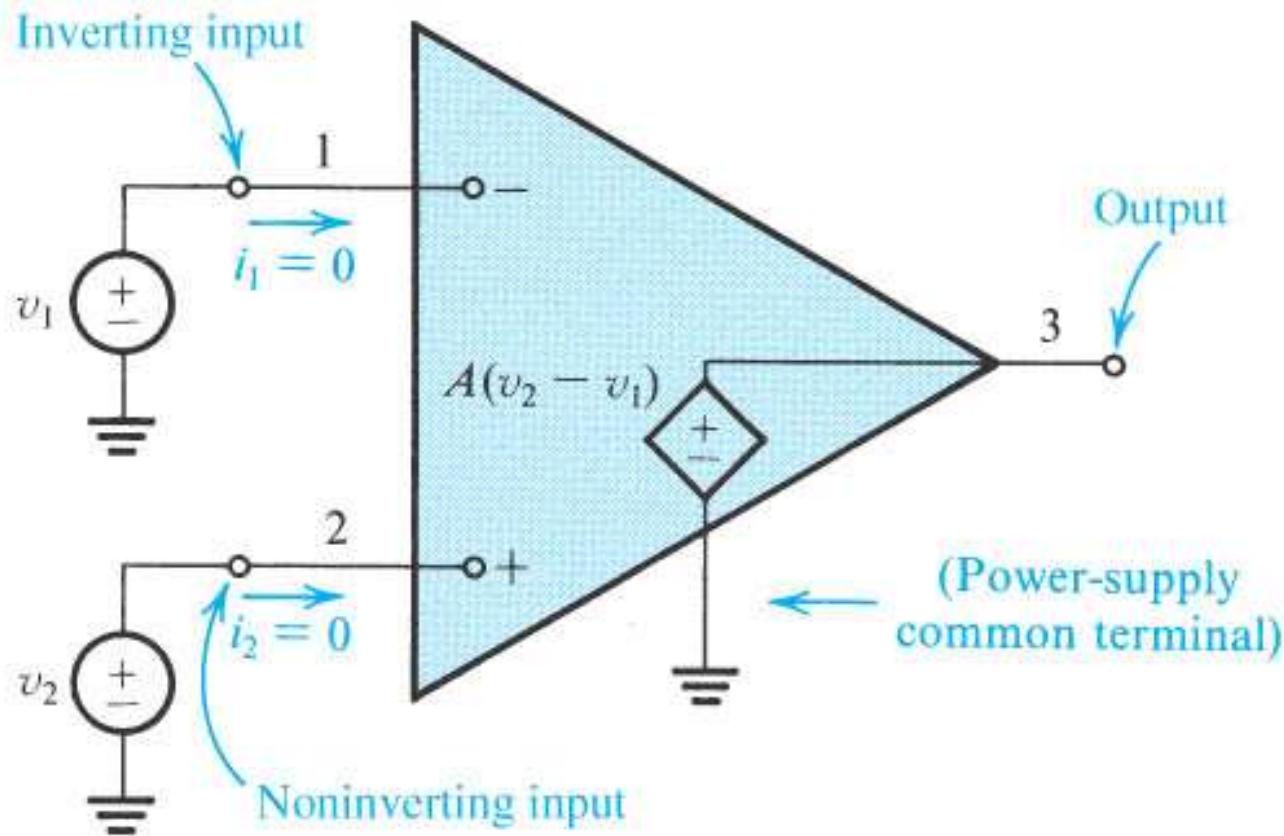



# Virtual Short

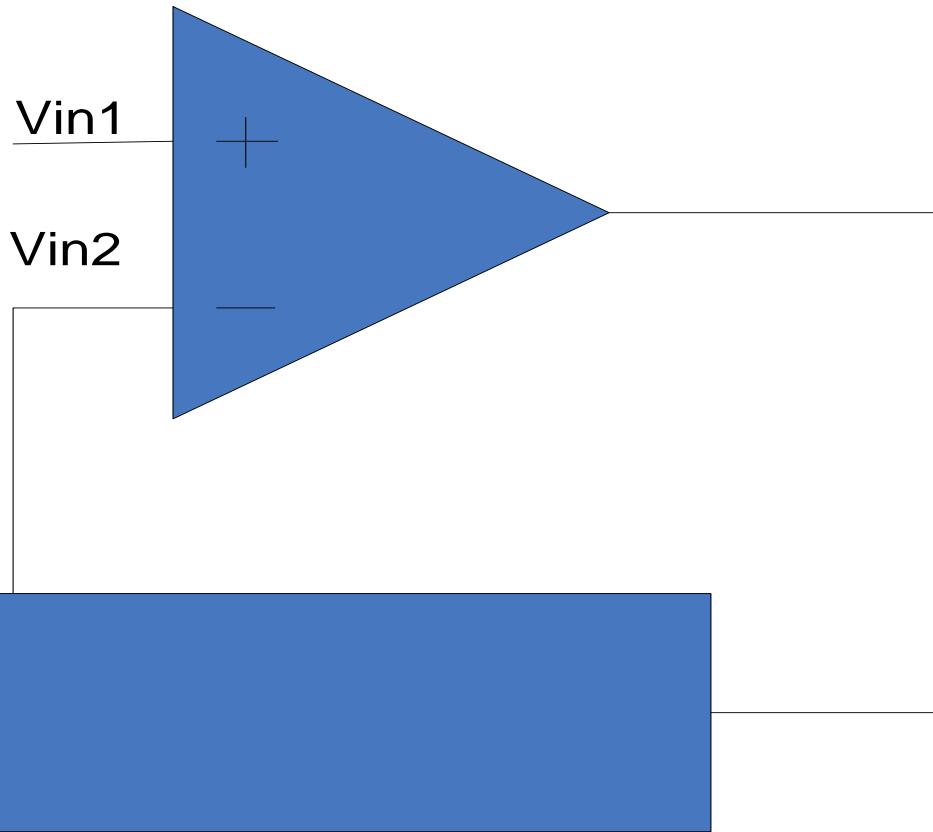


$$V^- \approx V^+$$

$$I_{in1} = I_{in2} \approx 0$$

- Due to infinite gain of op amp, the circuit forces  $V_{in2}$  to be close to  $V_{in1}$ , thus creating a virtual short.



# Unity Gain Amplifier

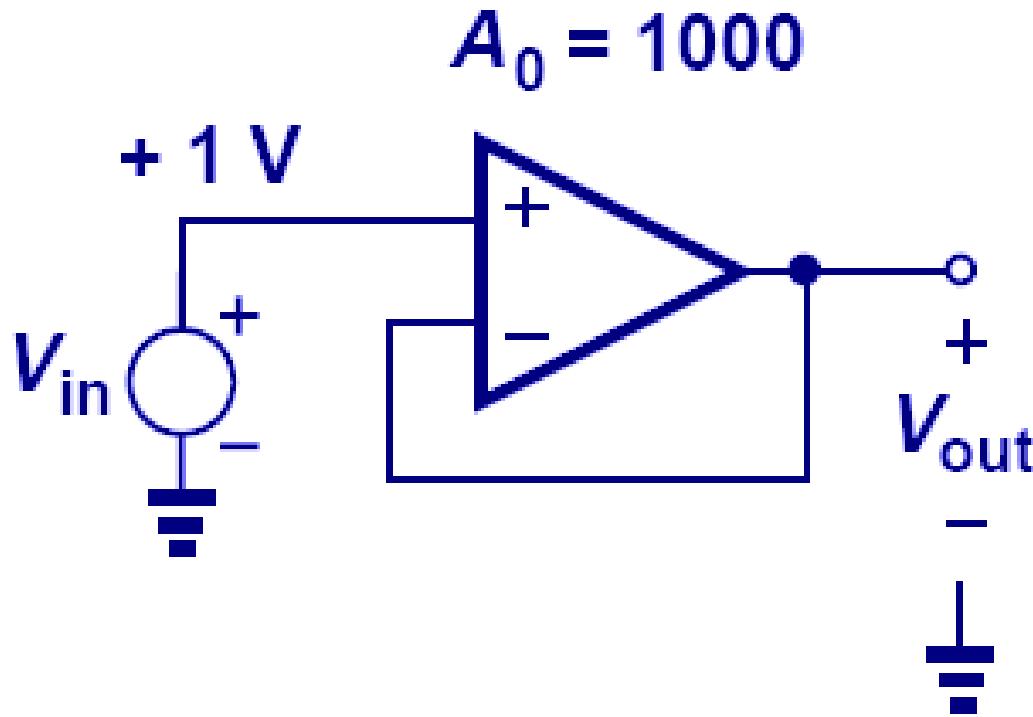


$$V_{out} = A_0(V_{in1} - V_{in2}) \\ = A_0(V_{in} - V_{out}).$$

$$V_{out} = A_0 (V_{in} - V_{out})$$

$A_0 = 1000$ ,  $V_{in} = 1$  V, and  $V_{out} = 0.999$  V.



# Op Amp with Supply Rails

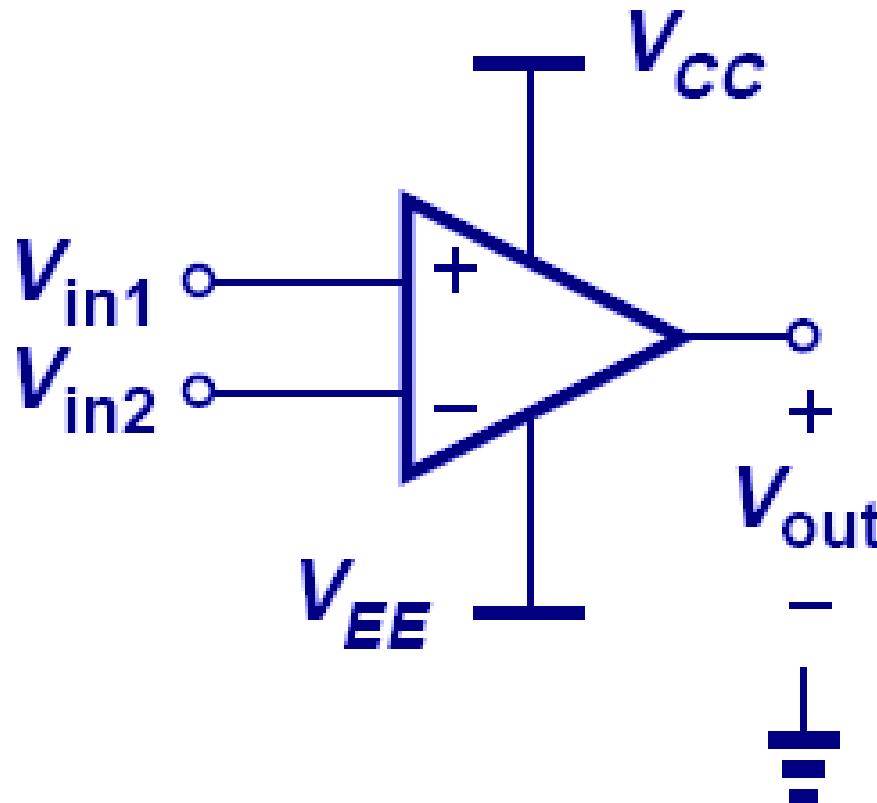


- To explicitly show the supply voltages,  $V_{cc}$  and  $V_{EE}$  are shown.
- In some cases,  $V_{EE}$  is zero.




# Op Amp with Supply Rail

اتٹاکوہستان دلوجھان

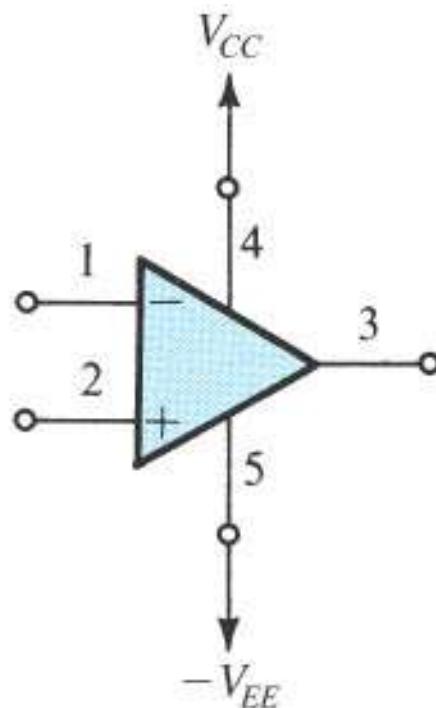


(a)

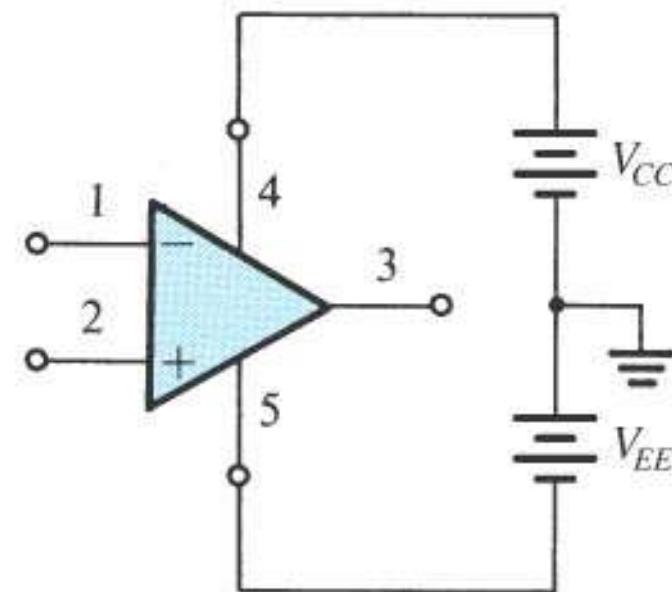

(b)
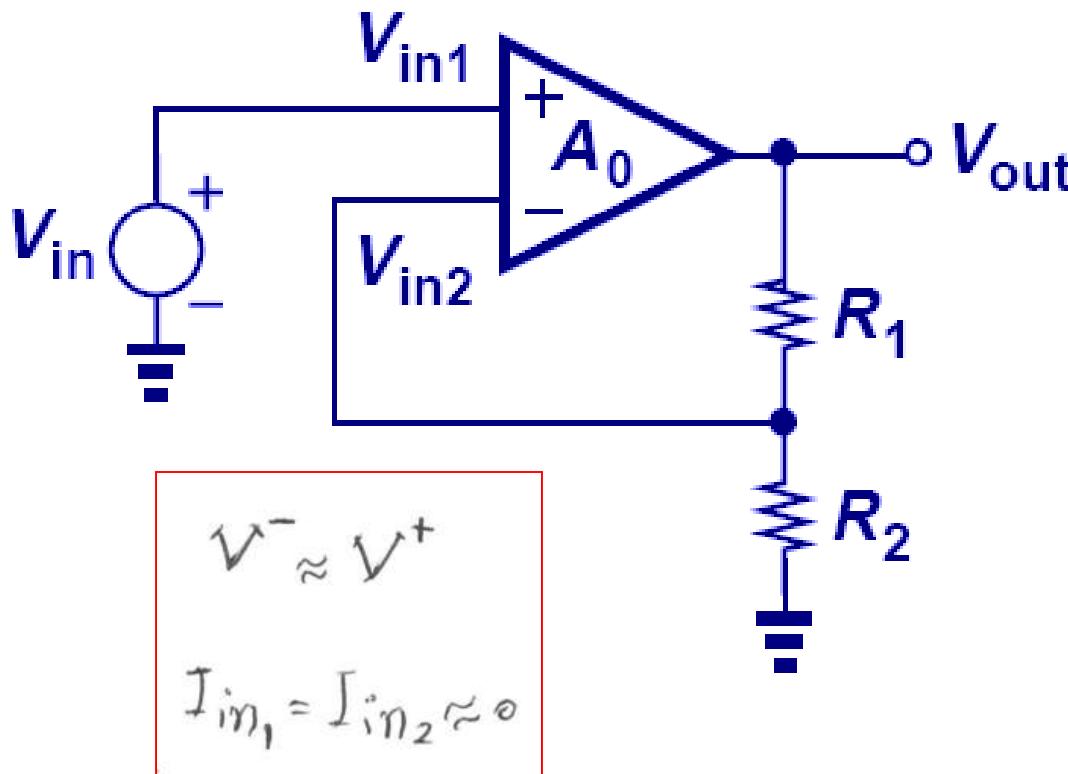
# Noninverting Amplifier (Infinite $A_o$ )



$$V_{in2} = \frac{R_2}{R_1 + R_2} V_{out}$$

$$V_{in1} \approx V_{in2}$$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

- A noninverting amplifier returns a fraction of output signal thru a resistor divider to the negative input.
- With a high  $A_o$ ,  $V_{out}/V_{in}$  depends only on ratio of resistors, which is very precise.




## Noninverting Amplifier (Finite $A_0$ )

دانشگاه تهران، اسلامی

$$(V_{in1} - V_{in2})A_0 = V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{R_2}{R_1 + R_2}A_0}.$$

$$A_0 R_2 / (R_1 + R_2) \gg 1$$


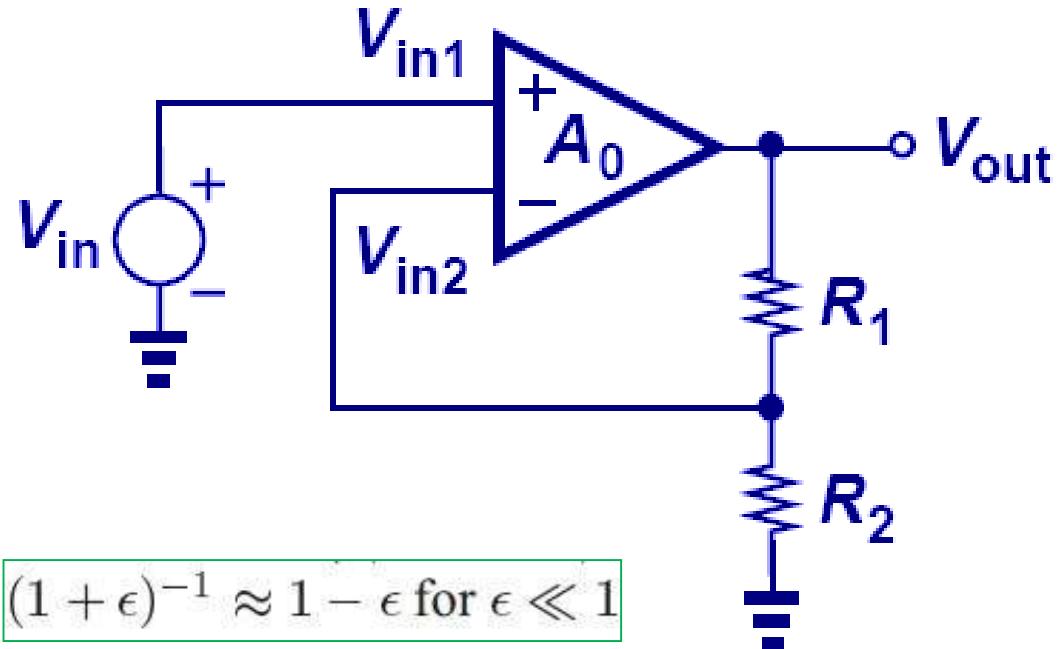


$$(1 + \epsilon)^{-1} \approx 1 - \epsilon \text{ for } \epsilon \ll 1$$

$$\frac{V_{out}}{V_{in}} \approx \left(1 + \frac{R_1}{R_2}\right) \left[ 1 - \left(1 + \frac{R_1}{R_2}\right) \frac{1}{A_0} \right]$$

➤ The error term indicates the larger the closed-loop gain, the less accurate the circuit becomes.
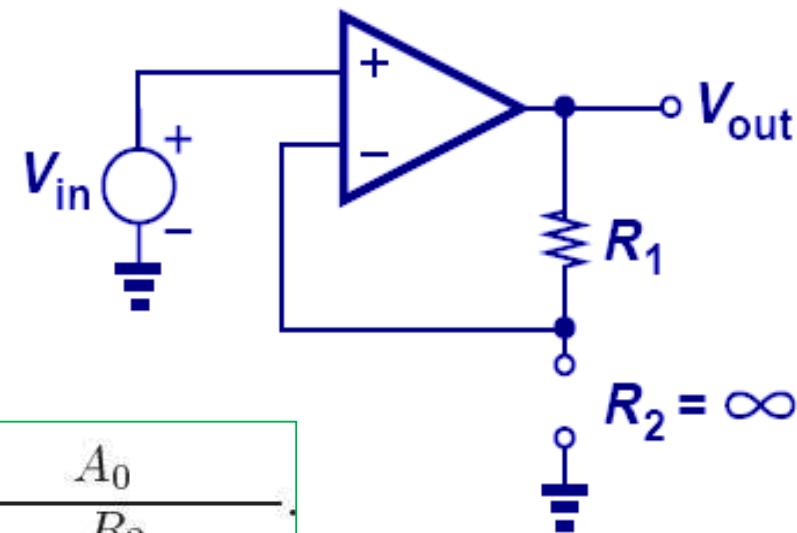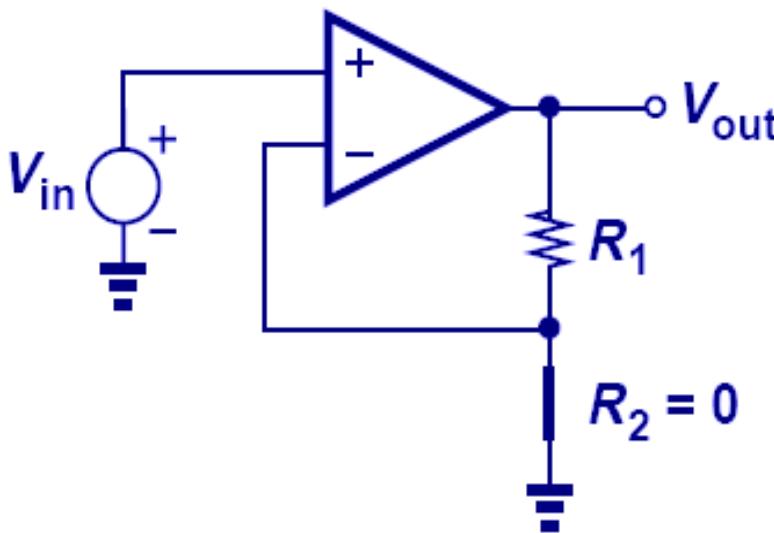
## Example 8.2: Extreme Cases of $R_2$ (Infinite $A_0$ )




$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0}$$


- If  $R_2$  is zero, the loop is open and  $V_{out}/V_{in}$  is equal to the intrinsic gain of the op amp.
- If  $R_2$  is infinite, the circuit becomes a unity-gain amplifier and  $V_{out}/V_{in}$  becomes equal to one.




# Inverting Amplifier

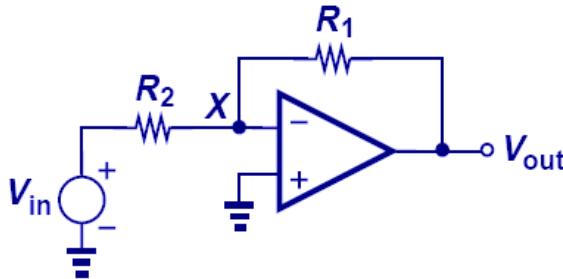

(a)

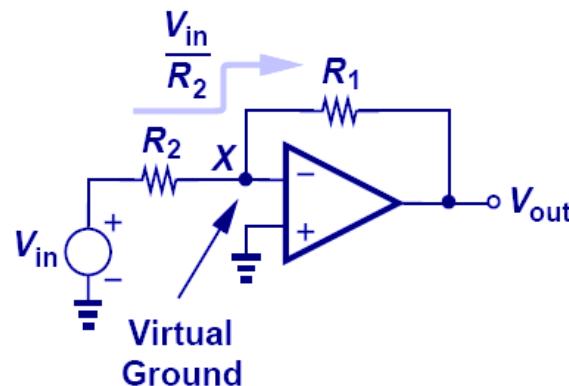

(b)

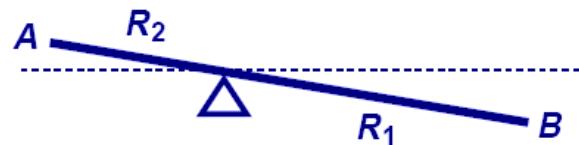

(c)

$$V^- \approx V^+$$

$$I_{in1} = I_{in2} \approx 0$$



$$\frac{0 - V_{out}}{R_1} = \frac{V_{in}}{R_2}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_1}{R_2}$$

➤ Infinite  $A_0$  forces the negative input to be a virtual ground.



# Inverting Amplifier

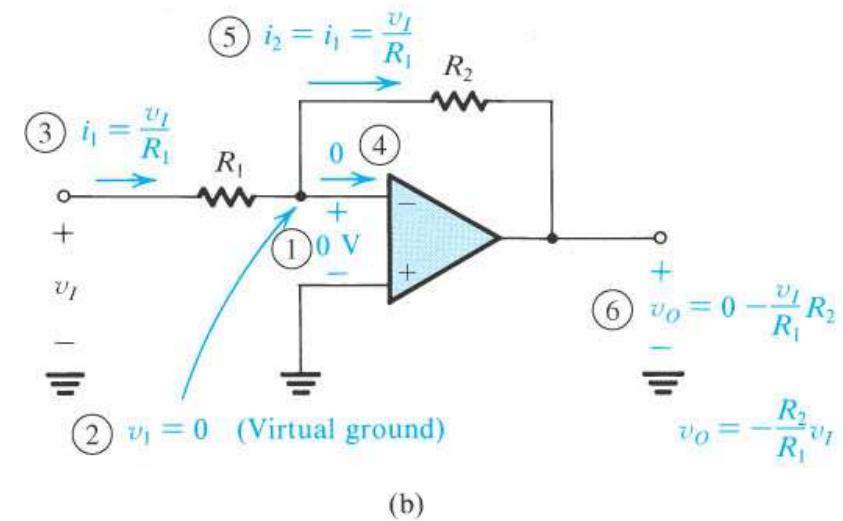
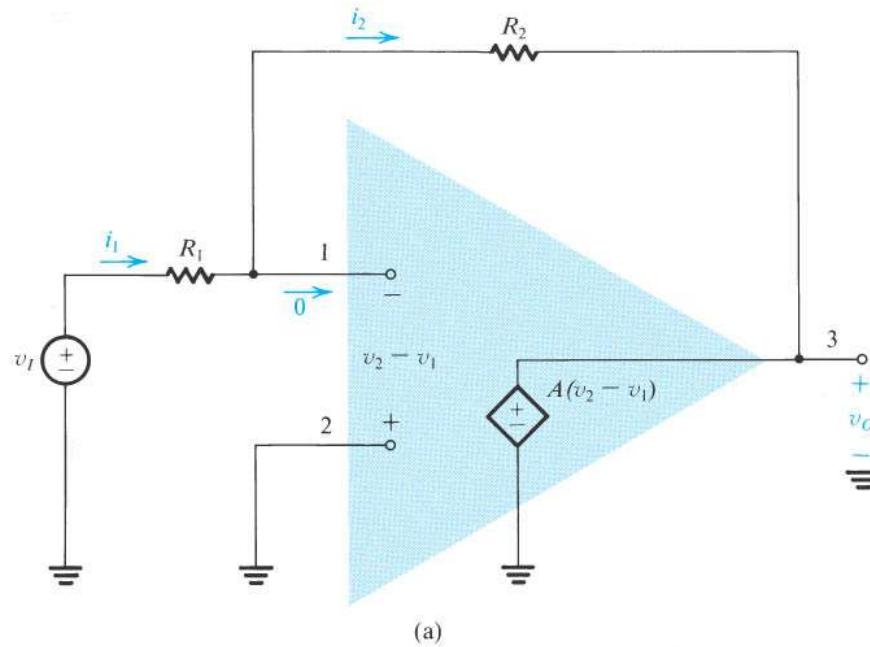


$$V^- \approx V^+$$

$$I_{in1} = I_{in2} \approx 0$$



## Another View of Inverting Amplifier

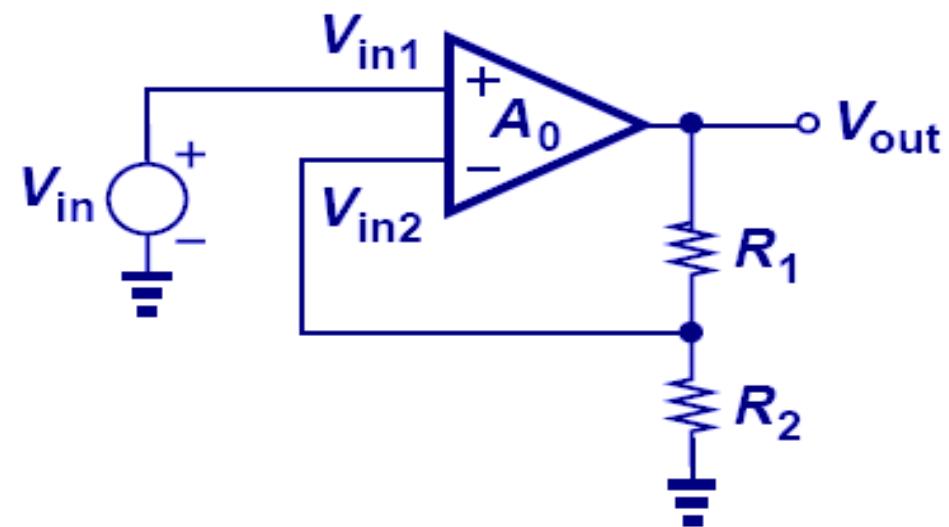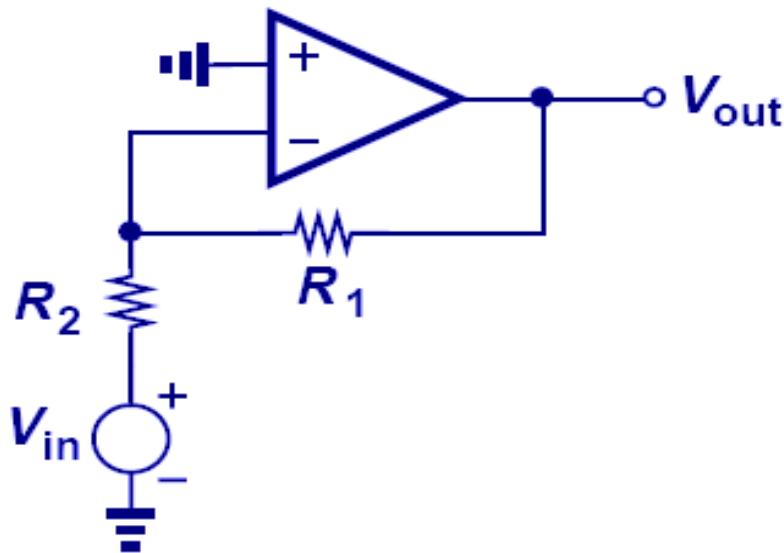

$$\frac{V_{out}}{V_{in}} = \frac{-R_1}{R_2}$$


**Inverting**

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

**Noninverting**



## Gain Error Due to Finite $A_0$

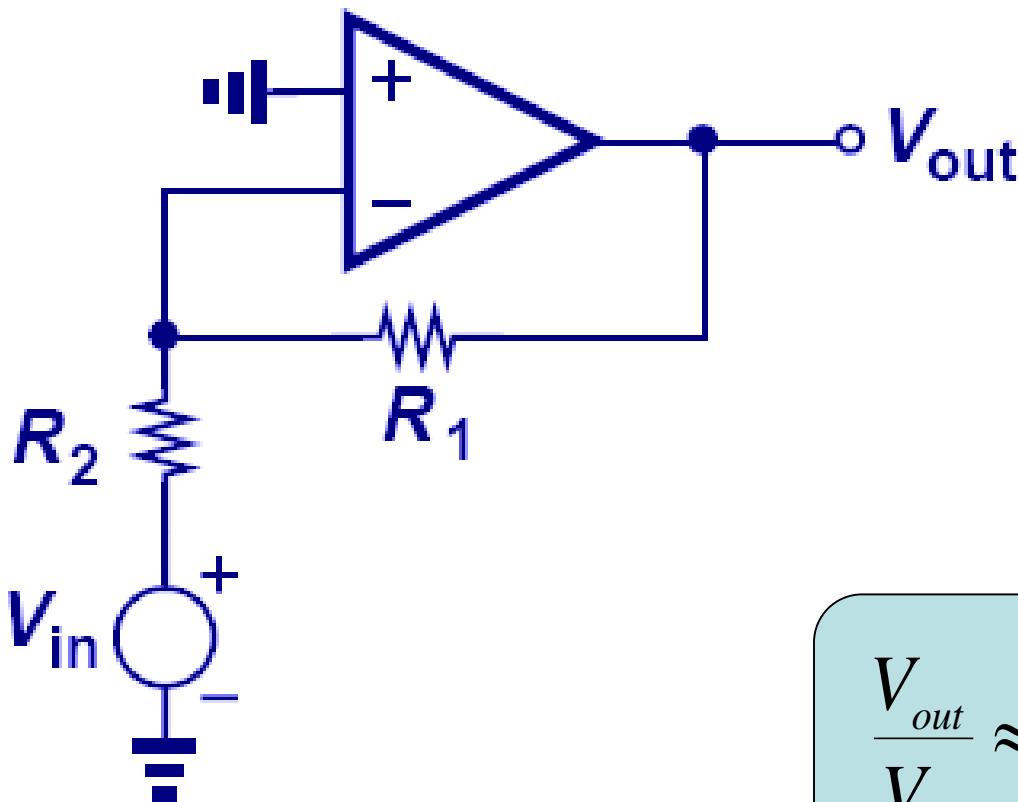


$$\begin{aligned}V_{out} &= A_0(V_{in1} - V_{in2}) \\&= -A_0 V_X.\end{aligned}$$

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= -\frac{1}{\frac{1}{A_0} + \frac{R_2}{R_1}(\frac{1}{A_0} + 1)} \\&= -\frac{1}{\frac{R_2}{R_1} + \frac{1}{A_0}(1 + \frac{R_2}{R_1})}.\end{aligned}$$

$$\frac{V_{out}}{V_{in}} \approx -\frac{R_1}{R_2} \left[ 1 - \frac{1}{A_0} \left( 1 + \frac{R_1}{R_2} \right) \right]$$

➤ The larger the closed loop gain, the more inaccurate the circuit is.



# Complex Impedances Around the Op Amp

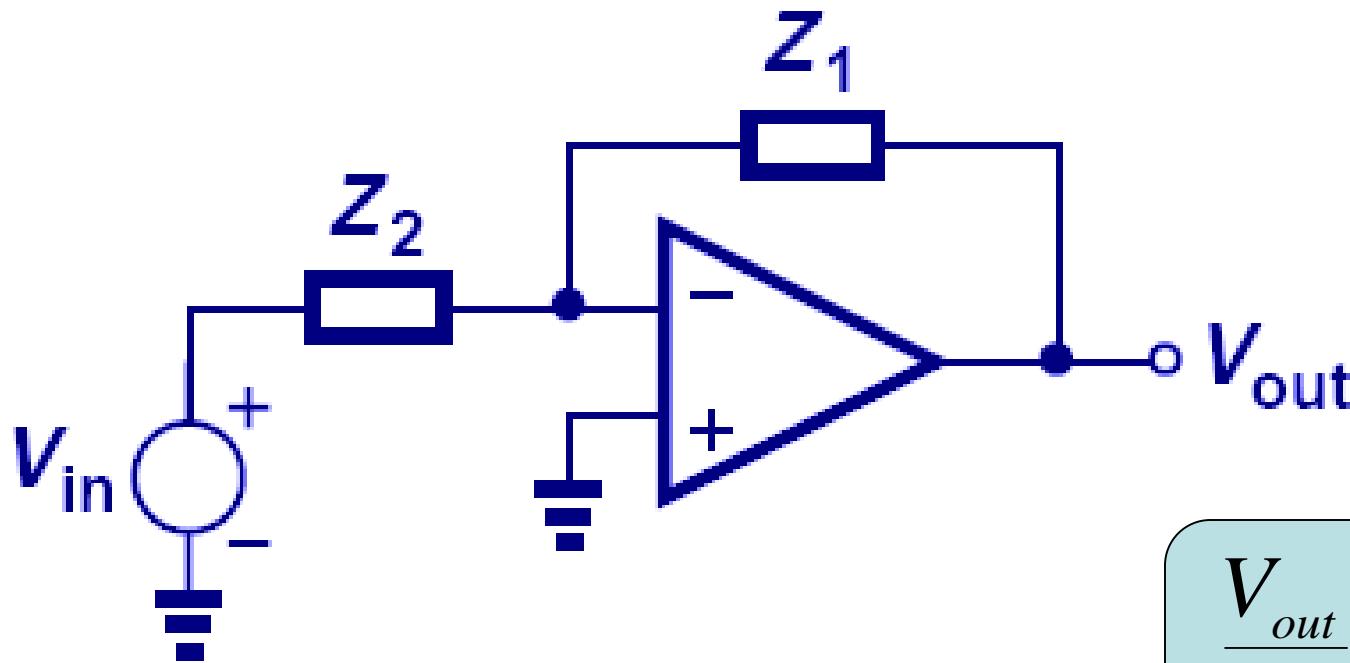

$$\frac{V_{out}}{V_{in}} \approx -\frac{Z_1}{Z_2}$$

- The closed-loop gain is still equal to the ratio of two impedances.

# Integrator

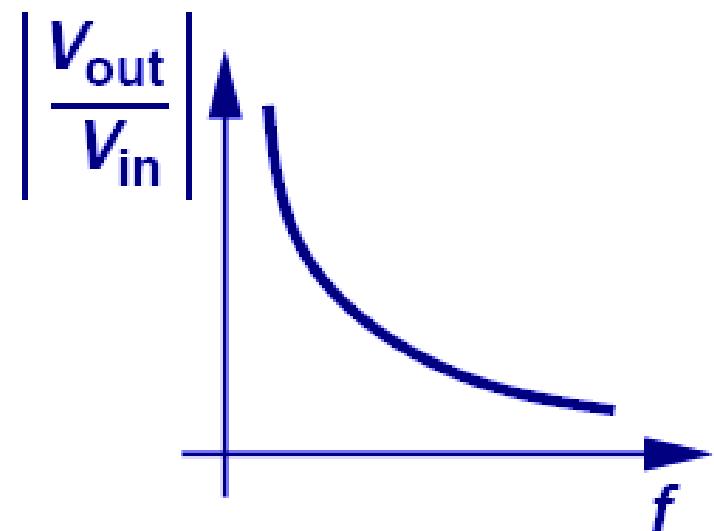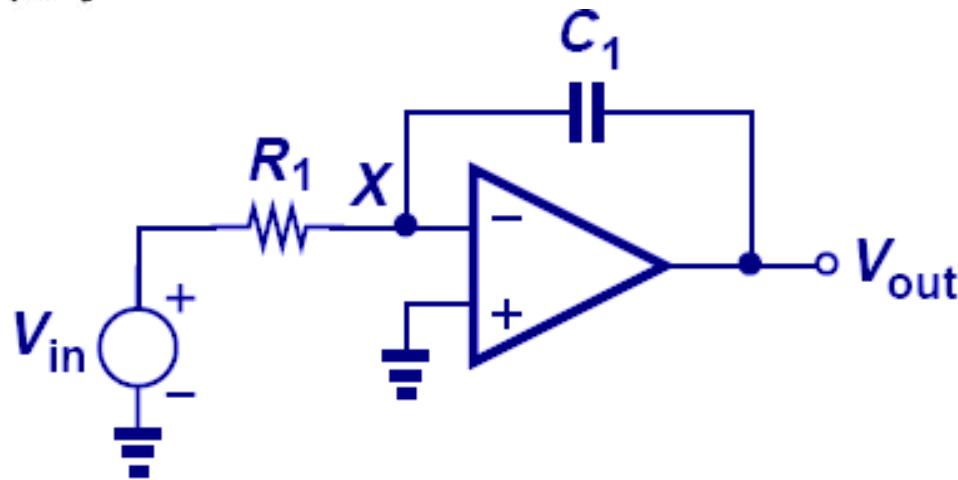



$$\frac{V_{out}}{V_{in}} = -\frac{1}{R_1 C_1 s}$$

$$\frac{V_{in}}{R_1} = -C_1 \frac{dV_{out}}{dt}$$

$$\frac{V_{out}}{V_{in}} = -\frac{1}{R_1 C_1 s}$$



$$V_{out} = -\frac{1}{R_1 C_1} \int V_{in} dt$$
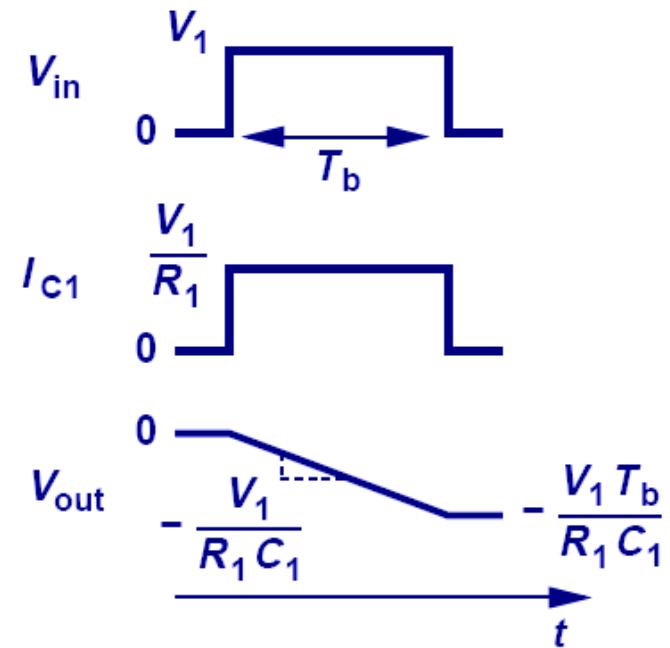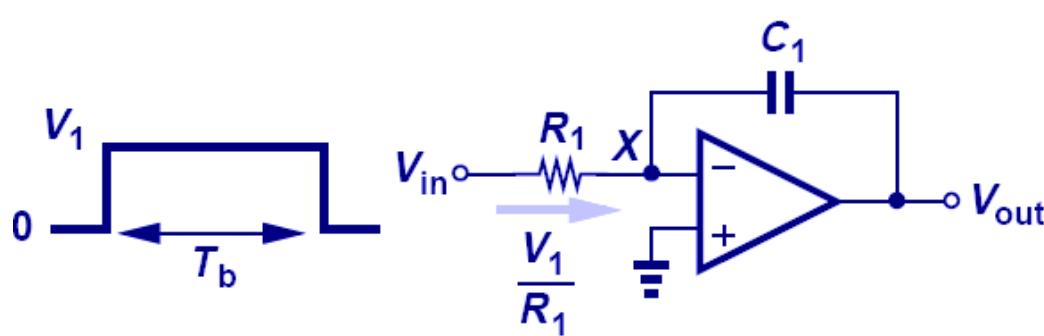
## Example 8.5: Integrator with Pulse Input




$$V_{\text{out}} = -\frac{1}{R_1 C_1} \int V_{\text{in}} dt = -\frac{V_1}{R_1 C_1} t \quad 0 < t < T_b$$
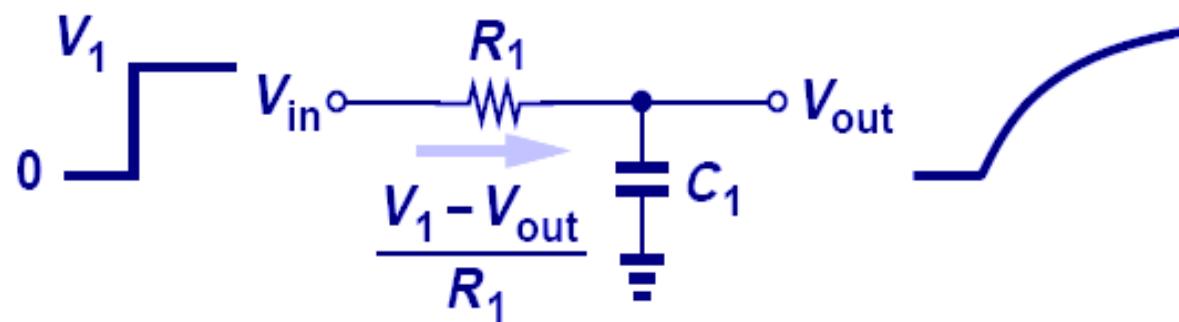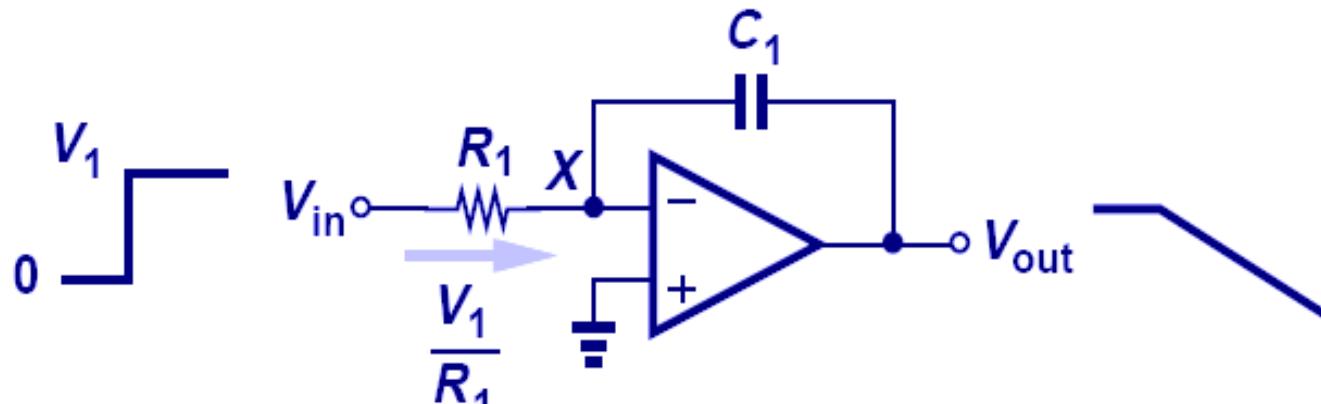
# Comparison of Integrator and RC Lowpass Filter



- The RC low-pass filter is actually a “passive” approximation to an integrator.
- With the RC time constant large enough, the RC filter output approaches a ramp.

# Lossy Integrator


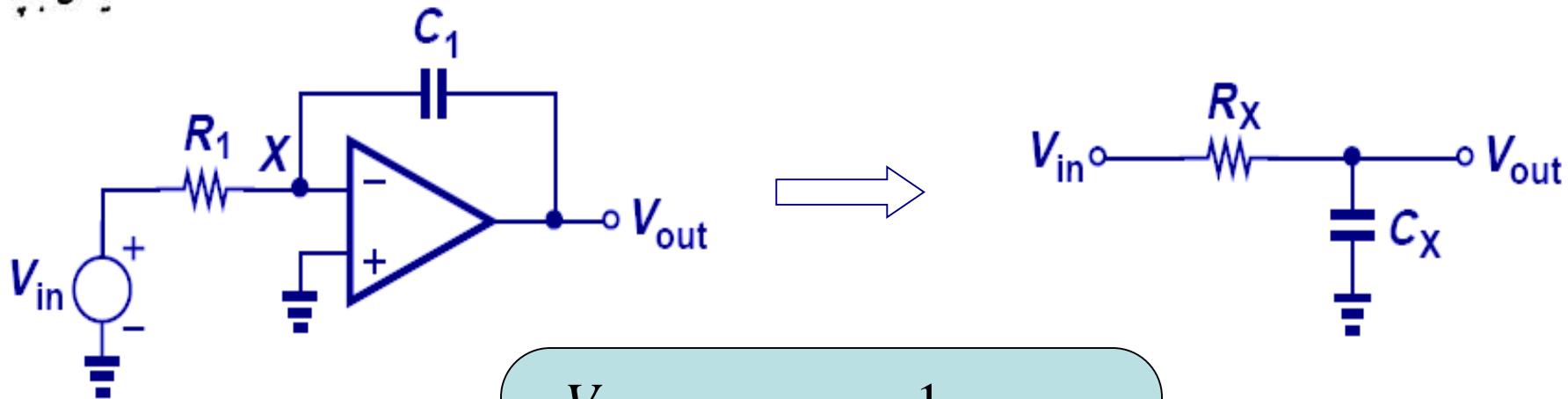


$$\frac{V_{out}}{V_{in}} = \frac{-1}{\frac{1}{A_0} + \left(1 + \frac{1}{A_0}\right)R_1 C_1 s}$$

- When finite op amp gain is considered, the integrator becomes lossy as the pole moves from the origin to  $-1/[(1+A_0)R_1C_1]$ .
- It can be approximated as an RC circuit with C boosted by a factor of  $A_0+1$ .




# Differentiator

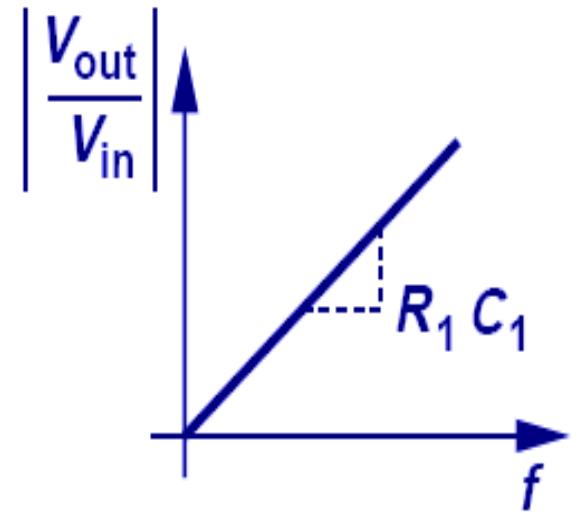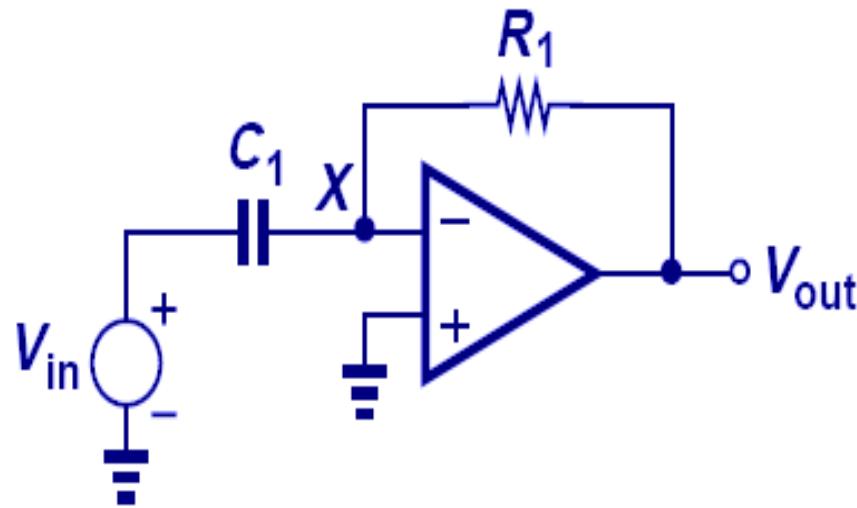

$$V_{out} = -R_1 C_1 \frac{dV_{in}}{dt}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_1}{1} = -R_1 C_1 s$$
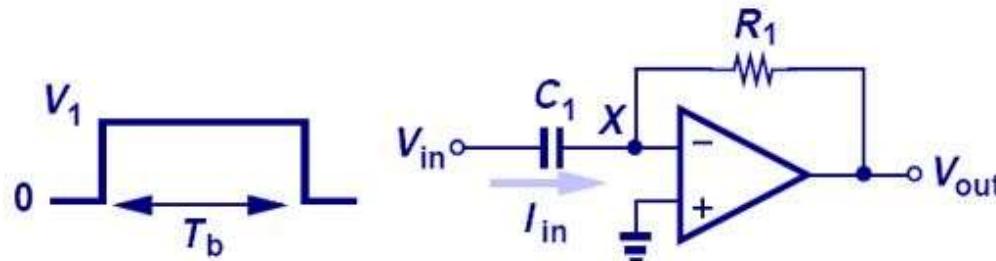
## Example 8.7: Differentiator with Pulse Input




$$I_{in} = C_1 \frac{dV_{in}}{dt} = C_1 V_1 \delta(t).$$

$$\begin{aligned} V_{out} &= -I_{in} R_1 \\ &= -R_1 C_1 V_1 \delta(t). \end{aligned}$$

$$\begin{aligned} I_{in} &= C_1 \frac{dV_{in}}{dt} \\ &= C_1 V_1 \delta(t). \end{aligned}$$

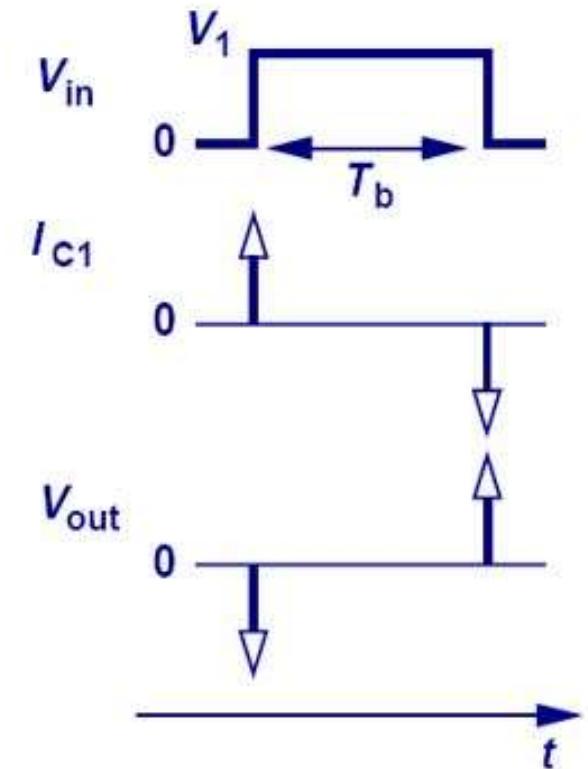
$$\begin{aligned} V_{out} &= -I_{in} R_1 \\ &= R_1 C_1 V_1 \delta(t). \end{aligned}$$




$$V_{out} = \mp R_1 C_1 V_1 \delta(t)$$


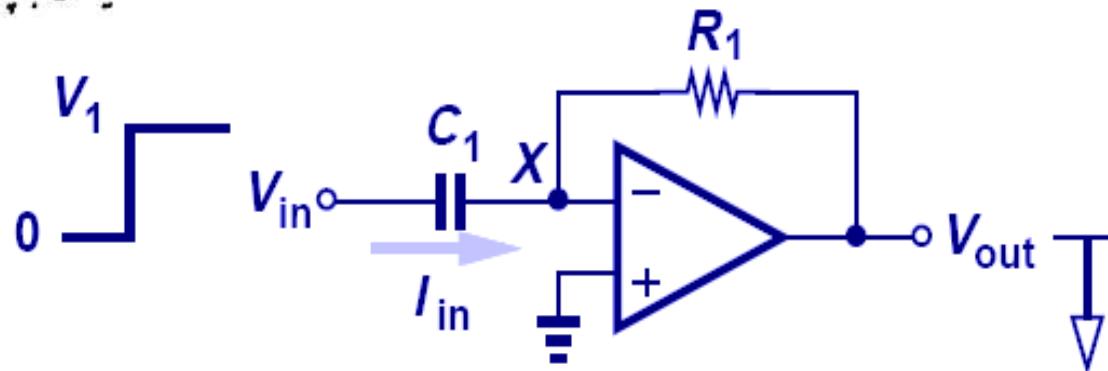
## Comparison of Differentiator and High-Pass Filter


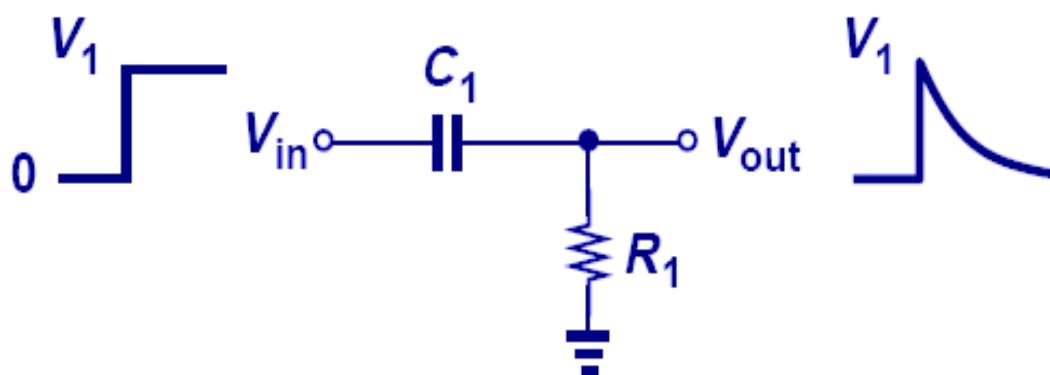
$$\frac{V_{in} - V_X}{\frac{1}{C_1 s}} = \frac{V_X - V_{out}}{R_1}.$$




$$\frac{V_{out}}{V_{in}} = \frac{-R_1 C_1 s}{1 + \frac{1}{A_0} + \frac{R_1 C_1 s}{A_0}}.$$

$$s_p = -\frac{A_0 + 1}{R_1 C_1}.$$

- The RC high-pass filter is actually a passive approximation to the differentiator.
- When the RC time constant is small enough, the RC filter approximates a differentiator.




## Lossy Differentiator

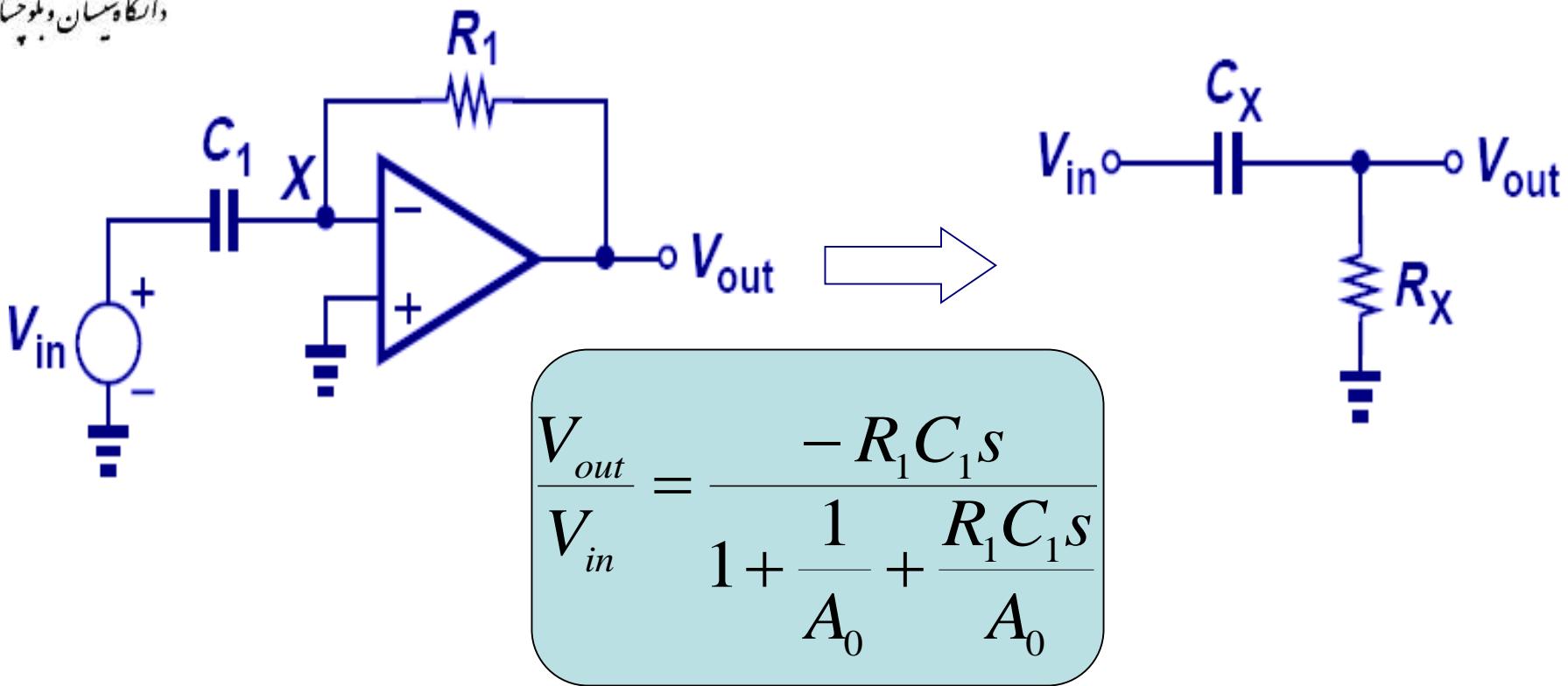

- When finite op amp gain is considered, the differentiator becomes lossy as the zero moves from the origin to  $-(A_0+1)/R_1 C_1$ .
- It can be approximated as an RC circuit with R reduced by a factor of  $(A_0+1)$ .

# Op Amp with General Impedances

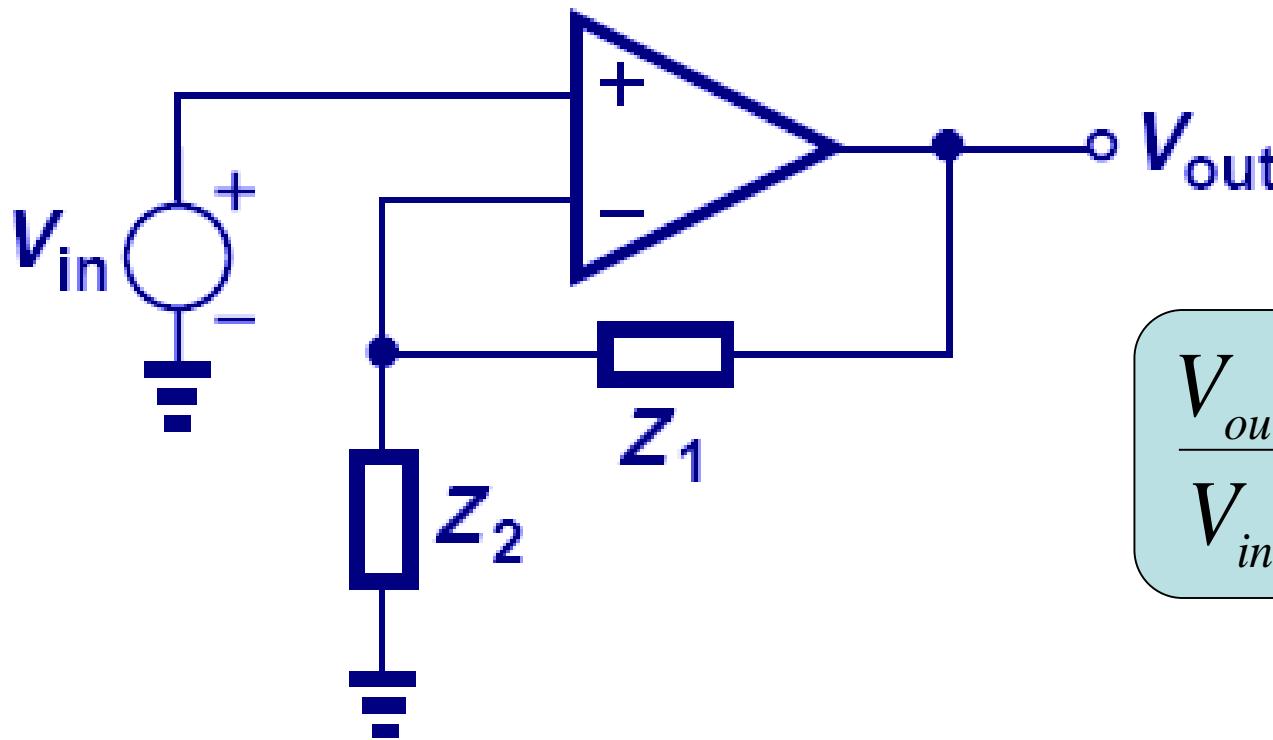


$$\frac{V_{out}}{V_{in}} = 1 + \frac{Z_1}{Z_2}$$

- This circuit cannot operate as ideal integrator or differentiator.



## Voltage Adder

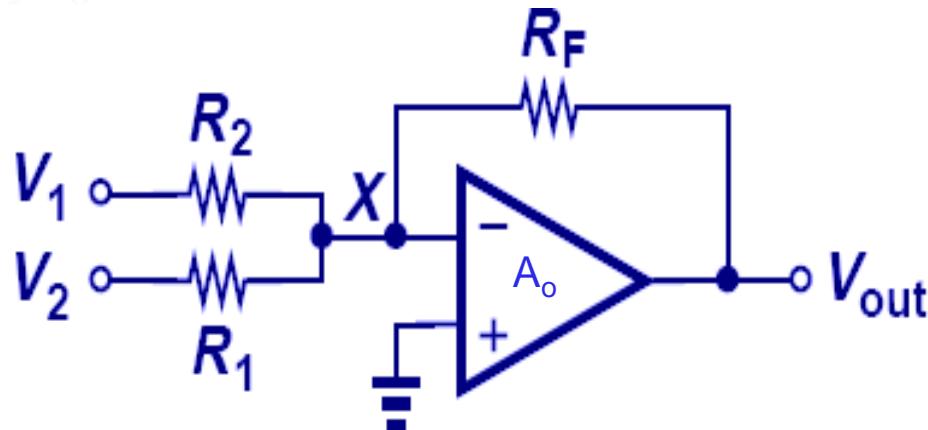

$$V^- \approx V^+$$

$$I_{in_1} = I_{in_2} \approx 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{-V_{out}}{R_F}.$$


$$V_{out} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$V_{out} = \frac{-R_F}{R} (V_1 + V_2)$$

If  $R_1 = R_2 = R$

- If  $A_o$  is infinite, X is pinned at ground, currents proportional to  $V_1$  and  $V_2$  will flow to X and then across  $R_F$  to produce an output proportional to the sum of two voltages.
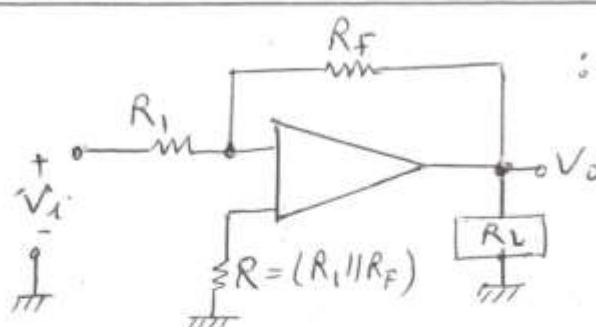
# صلح بخش اول - کاربردهای تقویت کننده هایی - ایجاد فرکانسی - غیر فرکانسی




۱ - تقویت کننده های (inverting Ampl.)

$$V_o = -\frac{R_F}{R_1} V_i \Rightarrow \frac{V_o}{V_i} = -\frac{R_F}{R_1}$$


$$R_i = \frac{V_i}{I_i} = R_1$$

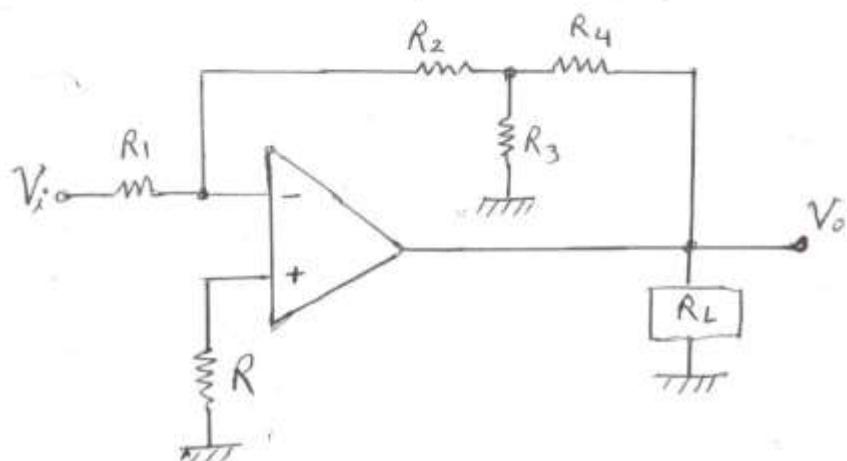- برای افزایش برد بیرون انتقامه از مقاومتی های (استفاده از سیم T می شود) :




$$\frac{V_o}{V_i} = \frac{-R_2}{R_1} \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

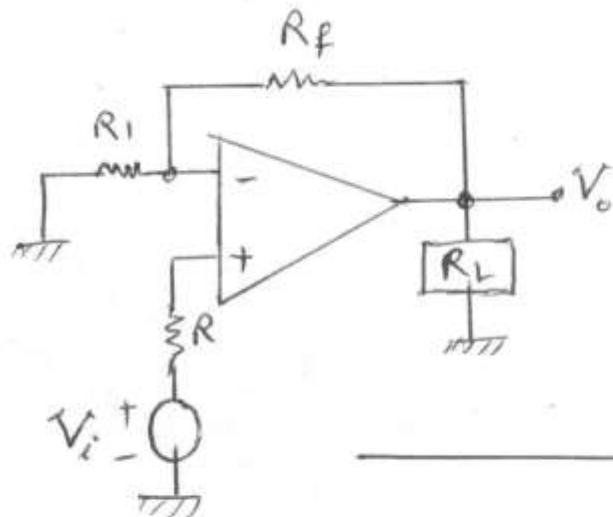برای حفظ سیم T رم (از مقاومت های  
ب ترکانس ۱/۰ درجه متر میگردد)



۱- تقویت کننده غیروارون (Non inverting )
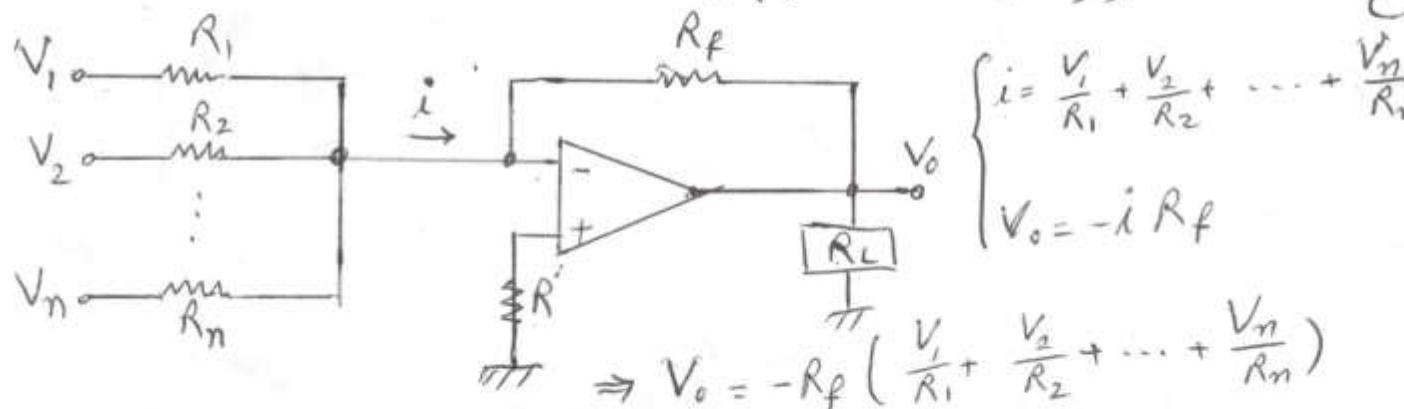
$$\frac{V_o}{V_i} = \left( 1 + \frac{R_f}{R_1} \right)$$



۲- تقویت کننده جمع سینه (Summing inverter )

$$\left\{ \begin{array}{l} i = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \\ V_o = -i R_f \end{array} \right.$$

$$\Rightarrow V_o = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

پس از:  $R_1 = R_2 = \dots = R_n = R \Rightarrow V_o = -\frac{R_f}{R} (V_1 + V_2 + \dots + V_n)$


۱) غش اول  $\Rightarrow$  کاربردهای تقویت کننده، مخلصه، جمع کننده - بفرز-تیترولگیک

۲- تقویت کننده متوسطگر و اردوگر :

$$R_f = \frac{R}{n} \xrightarrow{\text{ساده و بروز}} \text{در مکار جمع کننده وارونگر : اگر}$$


$$\Rightarrow V_o = - \left( \frac{V_1 + V_2 + \dots + V_n}{n} \right)$$

جمع کننده ناوارونگر (با بروز) - ۳

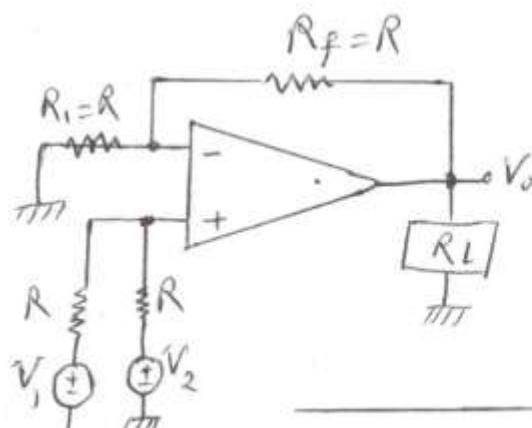


$$\begin{cases} V^+ = \frac{V_1 + V_2}{2} \\ V^- = V^+ \end{cases} \Rightarrow V_o = \left( 1 + \frac{R}{R} \right) V^+$$
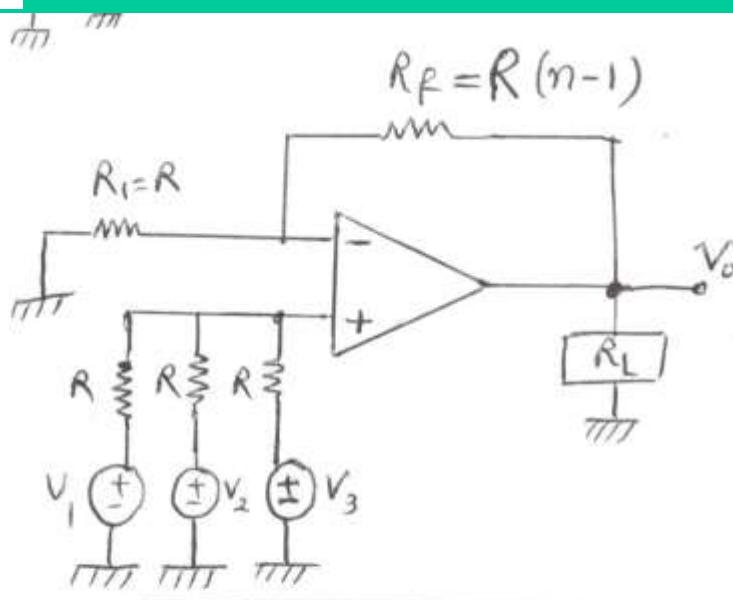
$$\Rightarrow V_o = 2 \left( \frac{V_1 + V_2}{2} \right) = V_1 + V_2$$



ویرانی و تغییرات
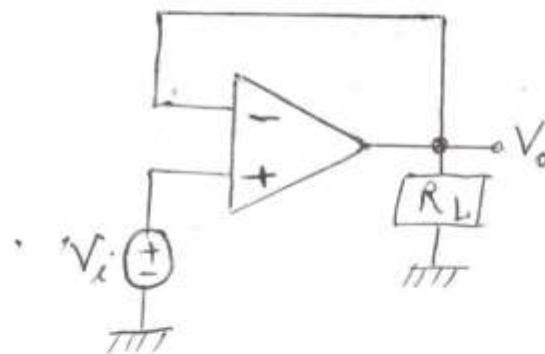
$$V^+ = \frac{1}{3}(V_1 + V_2 + V_3) \quad : \text{اگر}$$



(Voltage follower) ویرانی - V

(Source follower) ویرانی -

(Unity gain Amp.) ویرانی -

متصل میگیرد (یافر)

(Isolation Amp.) ویرانی -


$$V_o = V_x$$

$$\left\{ \begin{array}{l} R_i \uparrow, \text{Gain} = 1 \\ R_o \downarrow \end{array} \right\}$$



۳) محنت اول: مادر رهای تعریف کنند و مهملایت - تضليل و ایجاد متن

٨ - تعریف کنند؛ تفاسیر کنند. (تفاضلی) :

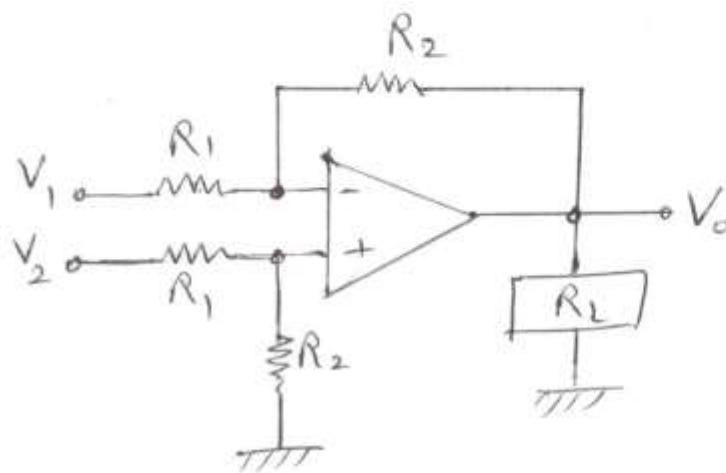


$$V_o = \left( \frac{R_2}{R_1} \right) (V_2 - V_1)$$

اہلیت: (بہرمن و گرماہرمن (۱۰) استفادہ)  
(نفع آثار منہجت)



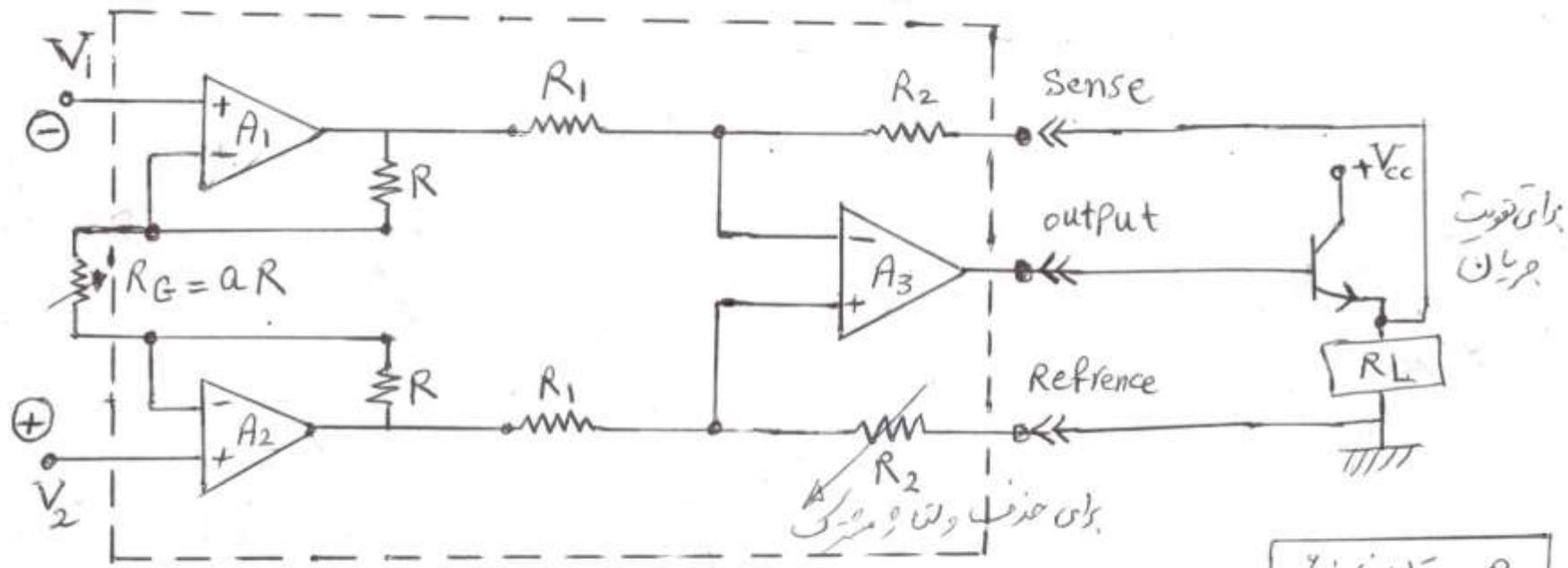
## ۹- تقویت کننده ایزوله دهنده (Instrumentation Amp. ) (نفاضنگی با فرودری) (AD524, AD624)



$$V_o = \left(1 + \frac{2R}{R_G}\right) \left(\frac{R_2}{R_1}\right) (V_2 - V_1) = \left(1 + \frac{2}{\alpha}\right) V_d$$

$$\left( \text{و: } R_2 = R_1, \quad R_G = \alpha R, \quad V_d = V_2 - V_1 \right)$$

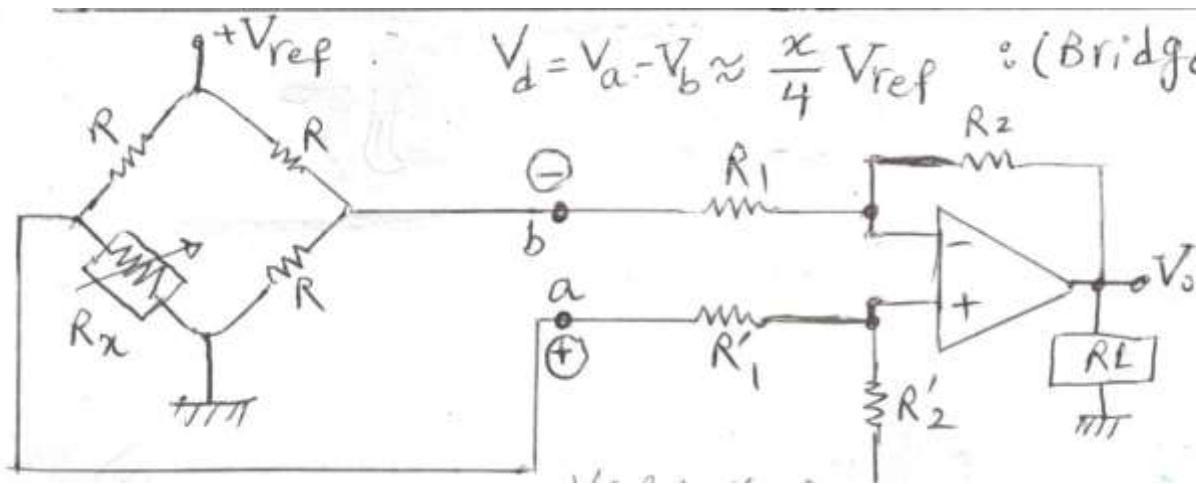میزانهای  $R_x$   
مسنور و ماتر اسند یزد  
سازمانهای علمی پژوهشی  
جهت است.



$$V_d = V_a - V_b \approx \frac{x}{4} V_{ref} \quad \text{(Bridge)}$$


$$R_x = R \pm \Delta R = R \left(1 \pm \frac{\Delta R}{R}\right) \\ = R (1+x)$$

$$\begin{cases} V_b = \frac{V_{ref}}{2} \\ V_a = \frac{1+x}{1+\frac{x}{2}} \cdot \frac{V_{ref}}{2} \end{cases}$$


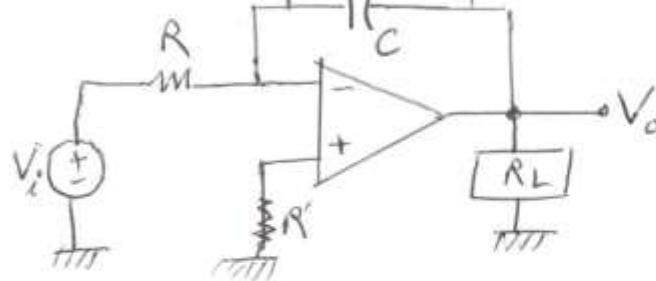
## دسته اول - کاربردهای تقریبی کنترل علیست - اندرال گیر و منطق گیر

۱۱- مدار اندرال گیر (واوفلر گیر) : [تبدیل سری به سری متعادل] (منظر پاسی نزدیک فرمان قطع صفر)



$$\frac{V_o}{V_i} = \frac{-1}{sCR} = \frac{-1}{j\omega CR}$$

\* برای اندرال گیر متعادل،  $RC$  باید خسین بزرگتر (از دوره تناوب سینال) و سری بود.

$$\therefore V_o(t) = V_c - \frac{1}{RC} \int_0^t V_i(t) dt$$

میتوان در فرمان مصنفر (dc) سه حافظه سار باز عمل کننده لذا بهره حلقه بسته می نماید خواهد شد.


برای اصلاح مدار اندرال گیر:  $\rightarrow$  با مداری کردن معاومنت بزرگ با حافظه اندرال گیر

ایضاً، رامکن (نیام دارد).

(نهایت اینجا، اندرال گیر را غیر (نیمه) کننده).


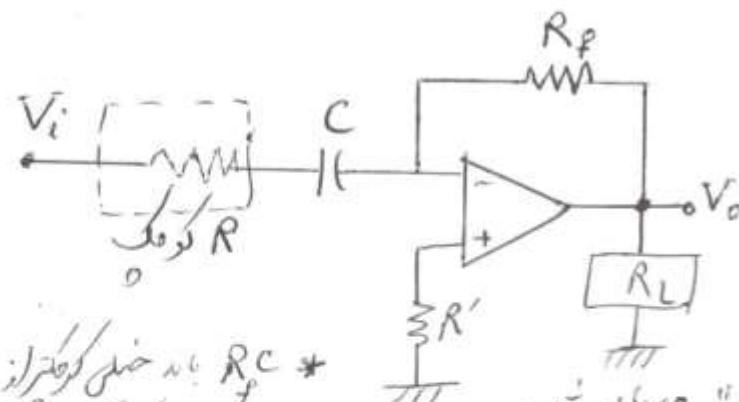
## ۱۲ - مدار متنق‌گیر (نیتر بالانس با مرکانس قطع‌نامه‌ور)



$$\frac{V_o}{V_i} = -SCR_f = -j\omega CR_f$$

$$\therefore V_o(t) = -R_f C \frac{dV_i}{dt}$$

حسن‌ساز آن مدار متنق‌گیر به "نیتر بالانس" نیز نویز می‌باشد. سینال ورودی باید سینال خنجر کوکتلز او را بسیار خنجر کرده باشد.


\* هر زمان که تغییر نماینده (Vi(t)) بوجود آید، در خروجی حسنه (جاید) می‌سرد.

+ در علی از مدارهای متنق‌گیر احتیاب می‌شود، و اگر انتقامه سرور، معمولاً لازم است

مکانیکی می‌باشد که ممکن با خازن سری می‌سرد.




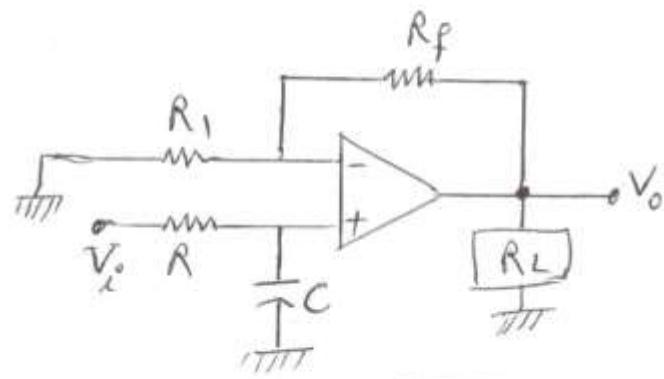۱۳- فیلتر اول- کاربرهای تقویت کننده معالج - فیلترهای معالج (active filter)



۱۳- فیلتر پایین گذر درج می‌کند :
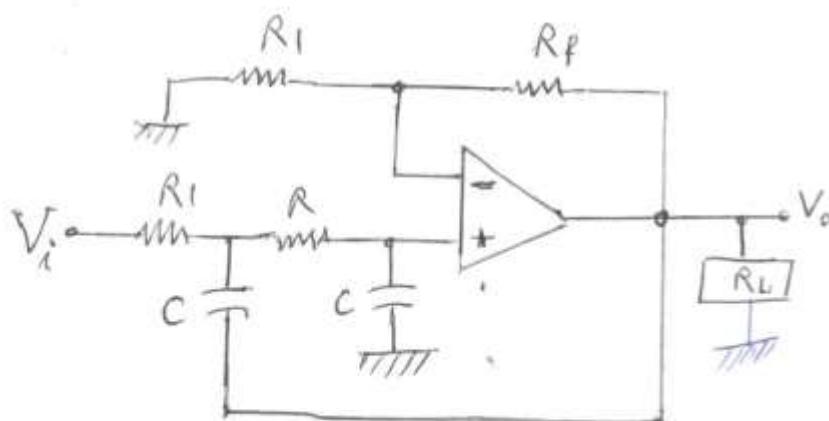
$$A_V(s) = \frac{V_o}{V_i} = \frac{R_1 + R_f}{R_1} \cdot \frac{1}{1 + SCR}$$



۱۴- فیلتر پایین گذر درج می‌کند :

$$A_{V_o} \triangleq 1 + \frac{R_f}{R_1}$$


$$A_V(s) = \frac{V_o}{V_i} = \frac{A_{V_o}}{(SCR)^2 + (3 - A_{V_o})SCR + 1}$$

۱۳ - فیلتر با سینک لذر درجه ۲ زوج: اگر در فیلتر با سینک لذر درجه دوم را بهم CasCode کنیم. فیلتر درجه ۲ زوج

بجست می‌کنیم و اگر از این طبق استفاده نمایم درجه سیم بجست می‌کنیم و ...

۱۴ - فیلتر با سینک لذر درجه ۲ فرد: اگر که فیلتر درجه ۲ که با یک فیلتر درجه دو باهم CasCode کنیم فیلتر با سینک لذر درجه ۲ فرد و اگر که فیلتر درجه ۲ که با ۲ دو فیلتر ریج درجه دو CasCode کنیم فیلتر با سینک لذر درجه ۲ فرد می‌گردیم.

۱۵ - فیلتر بالا لذر: (درجه ۱ کم)

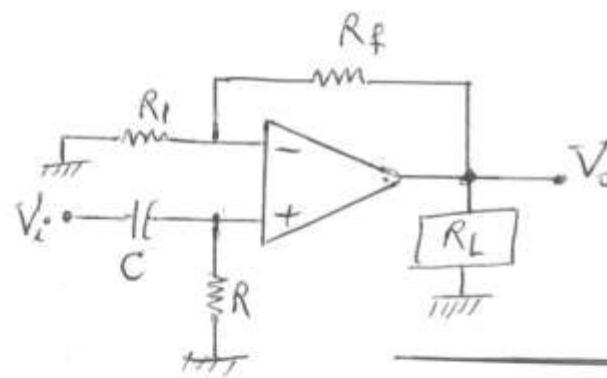


اگر جای خازن و مقاومت را در نظر نداشته باشیم عرضه کنیم  
تبدیل به فیلتر بالا لذر می‌شود.

$$A_V(s) = \frac{V_o}{V_i} = \left(1 + \frac{R_f}{R}\right) \frac{SCR}{1 + SCR}$$

۱۶ - فیلتر بالا لذر درجه ۲ دو:

$$A_{V_0} = 1 + \frac{R_f}{R_1}$$

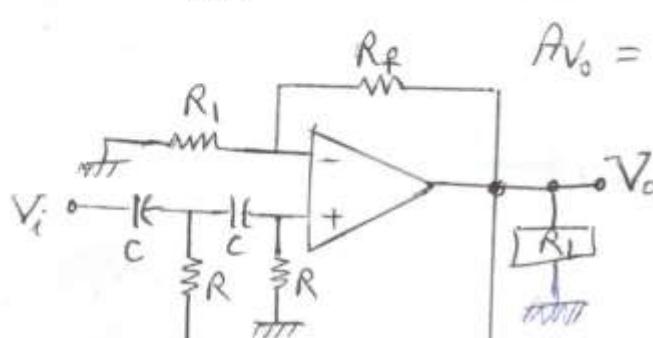

$$A_V(s) = \frac{A_{V_0}}{\left(\frac{1}{SCR}\right)^2 + (3 - A_{V_0})\left(\frac{1}{SCR}\right) + 1}$$





## الکترونیک ۲

فصل ۸ - تقویت کننده عملیاتی (آپ امپ)

قسمت دوم - کاربردهای غیرخطی

Mohammad Ali Mansouri- Birjandi


Majid Ghadrdan

Faculty of Electrical and Computer Engineering  
University of Sistan and Baluchestan (USB)

[mansouri@ece.usb.ac.ir](mailto:mansouri@ece.usb.ac.ir) ,  
[mamansouri@yahoo.com](mailto:mamansouri@yahoo.com)




# Precision Rectifier

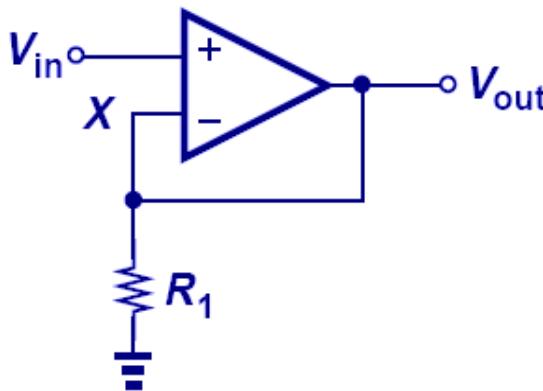


$$V^- \approx V^+$$

$$I_{in1} = I_{in2} \approx 0$$

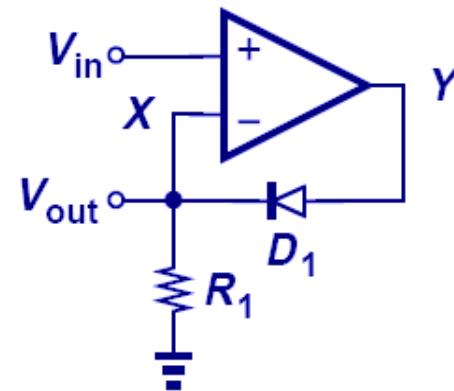

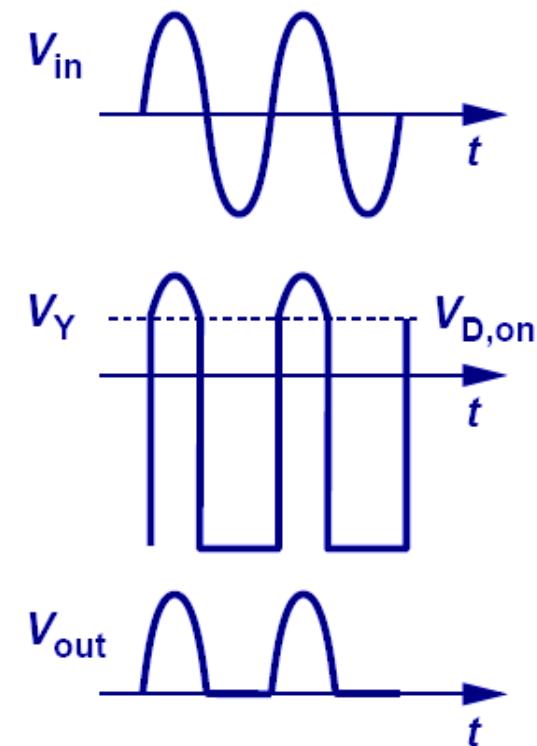فقط وقتی که دیود روشن هست، فیدیک برقرار است و میتوان از این فرضیات استفاده نمود.






- When  $V_{in}$  is positive, the circuit in b) behaves like that in a), so the output follows input.
- When  $V_{in}$  is negative, the diode opens, and the output drops to zero. Thus performing rectification.




نیش اول - کاربردهای تقویت کننده علیه ای - مکسیم کنندوها


۱۹ - مکسیم ساز موج رفیق

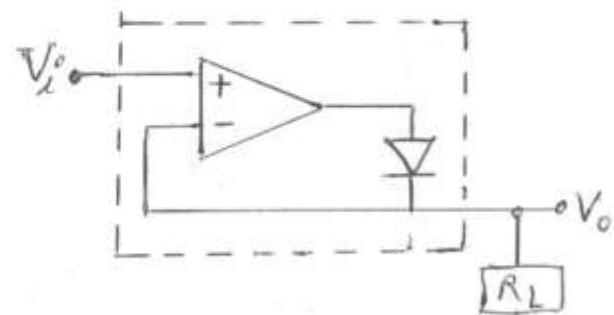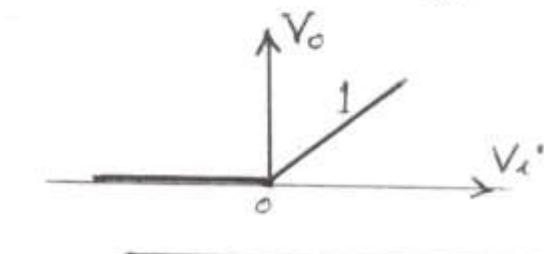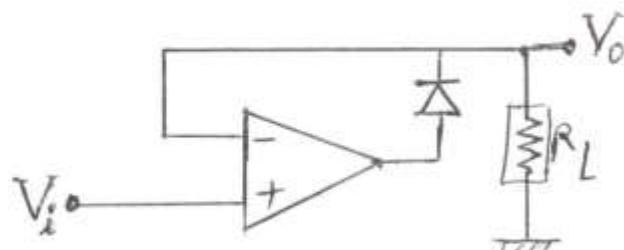
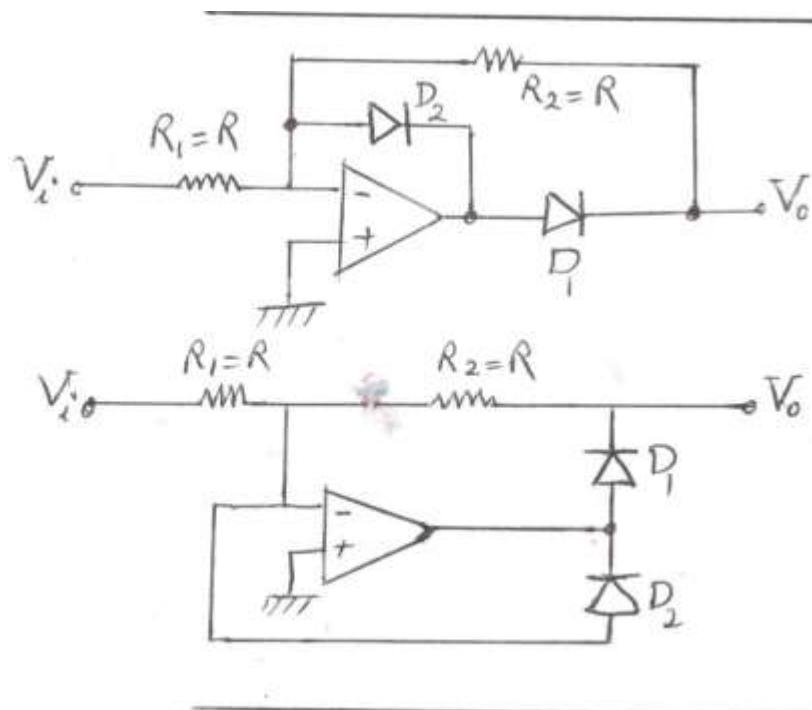
$$\begin{cases} V_i > 0 \Rightarrow D = on \Rightarrow V_0 = V_i & RL \\ V_i < 0 \Rightarrow D = off \Rightarrow V_0 = 0 & RL \end{cases}$$



نمودار موج دستگیری اصلی -  $V_o$

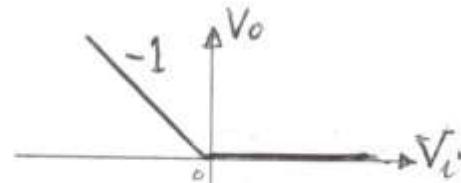


$$V_i > 0 \Rightarrow \begin{cases} D_1 = \text{OFF} \\ D_2 = \text{ON} \end{cases} \Rightarrow V_o = 0$$

$$V_i < 0 \Rightarrow \begin{cases} D_1 = \text{ON} \\ D_2 = \text{OFF} \end{cases} \Rightarrow V_o = -V_i$$




# Inverting Precision Rectifier

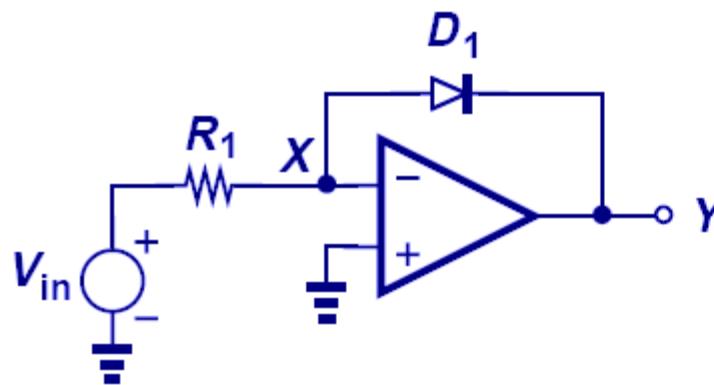


$$V^- \approx V^+$$

$$I_{in1} = I_{in2} \approx 0$$


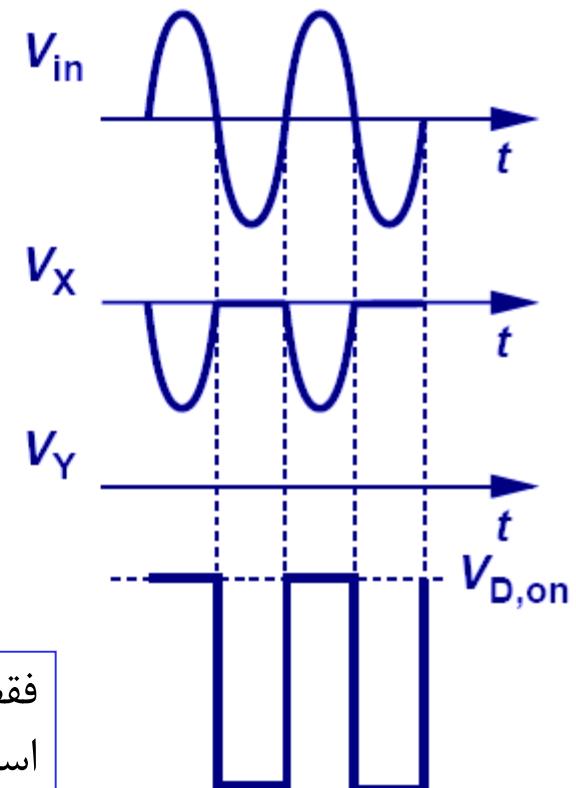
فقط وقتی که دیود روشن هست، فیدیک برقرار است و میتوان از این فرضیات استفاده نمود.



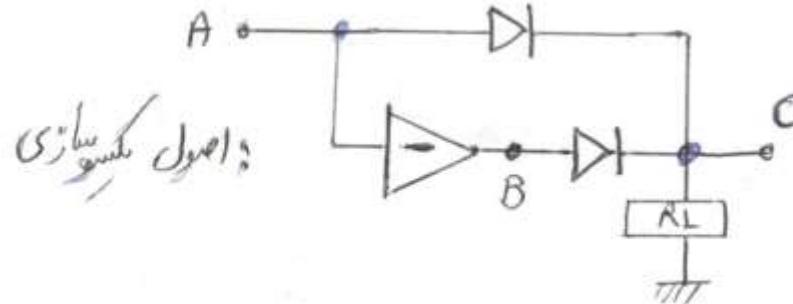
- When  $V_{in}$  is positive, the diode is on,  $V_y$  is pinned around  $V_{D, on}$ , and  $V_x$  at virtual ground.
- When  $V_{in}$  is negative, the diode is off,  $V_y$  goes extremely negative, and  $V_x$  becomes equal to  $V_{in}$ .



۲۱- نکسوساری موج دینامیک

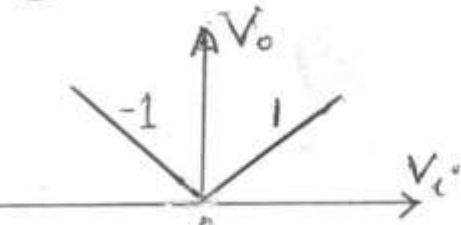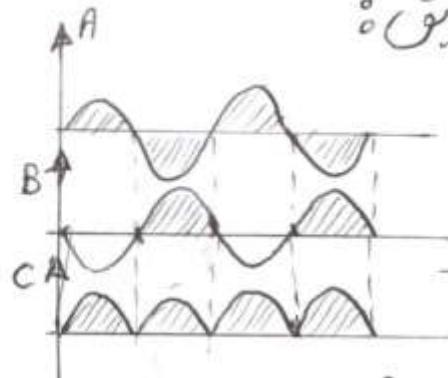
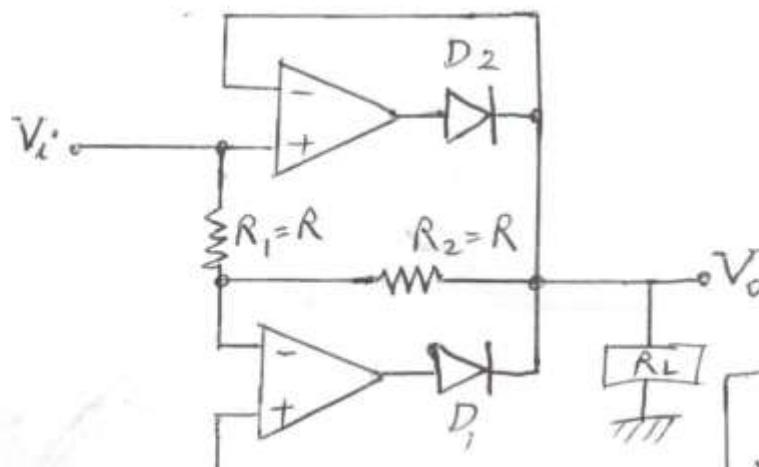
$$V_i > 0 \Rightarrow \begin{cases} D_2 = \text{ON} \\ D_1 = \text{OFF} \end{cases} \Rightarrow V_o = V_i$$











$$V_i < 0 \Rightarrow \begin{cases} D_1 = \text{ON} \\ D_2 = \text{OFF} \end{cases} \Rightarrow V_o = -V_i$$


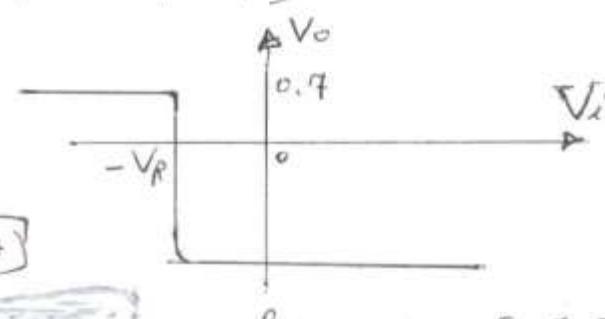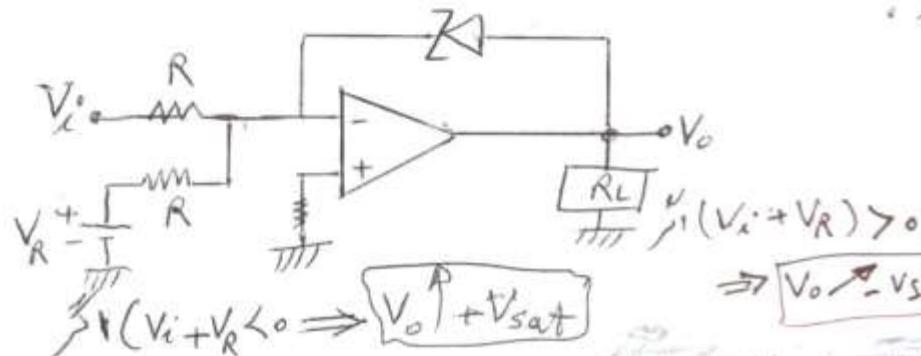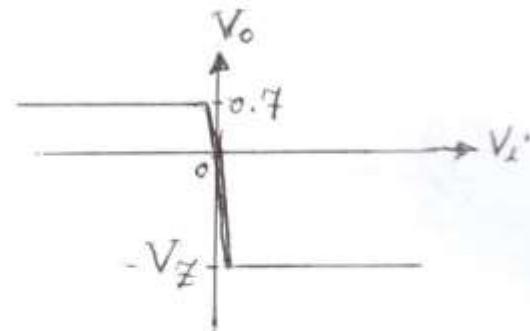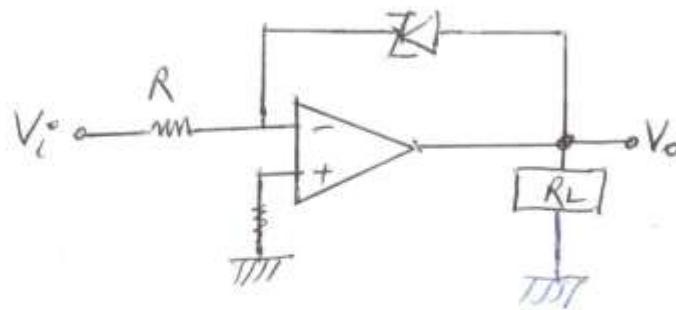
# ۳- بخش اول - کاربردهای تقویت کننده عملیاتی - تهییس کننده ها و میکرو کننده ها

- ۲۳ - دنگ راکتیو (متاسیم)، صفر ولت می باشد.




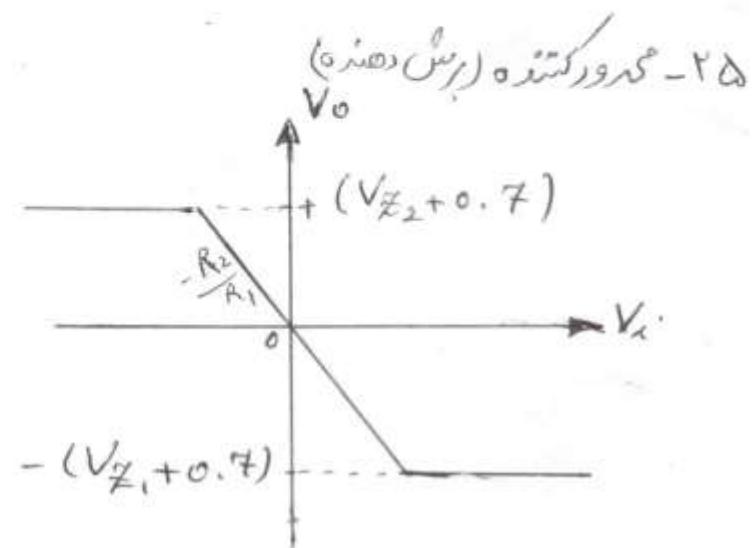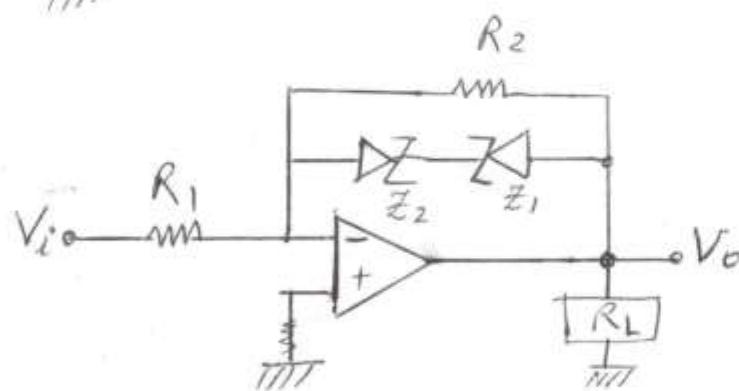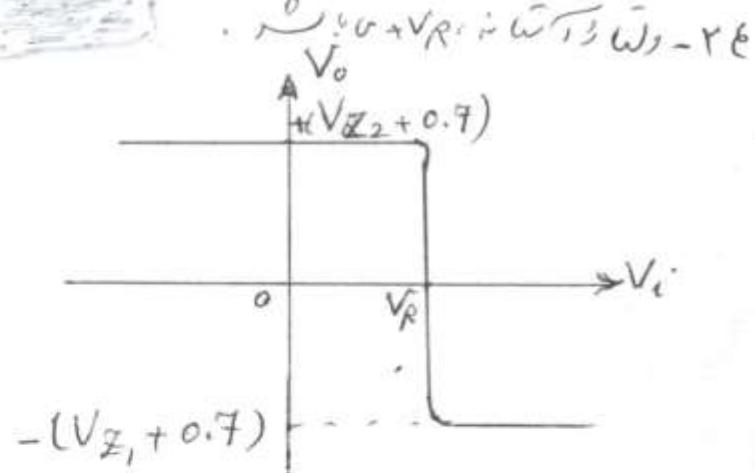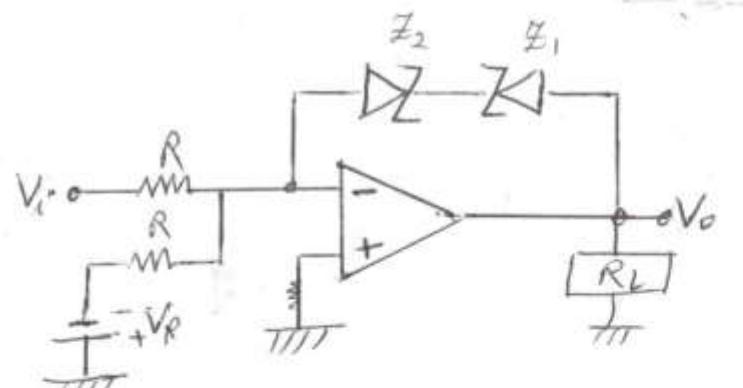




V-I-C

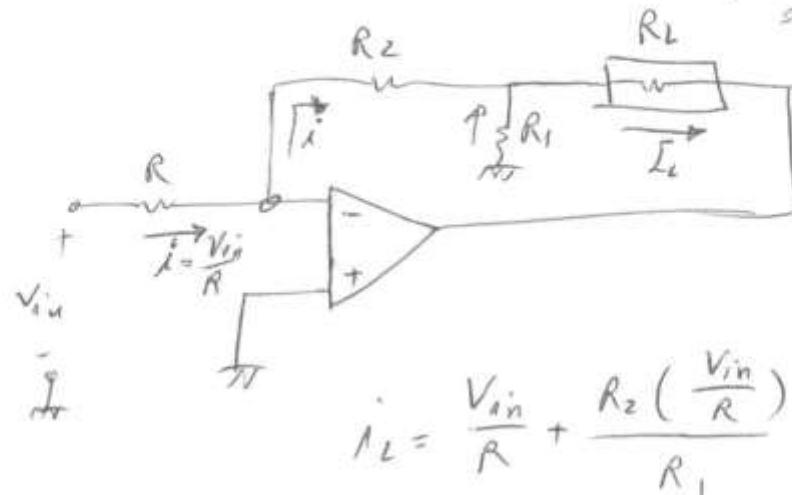محسن دوم - کاربرد مدارهای میخ هشت - مدل ول و برجیان



$$i_L = \frac{V_{in}}{R} \left( 1 + \frac{R_2}{R_1} \right)$$
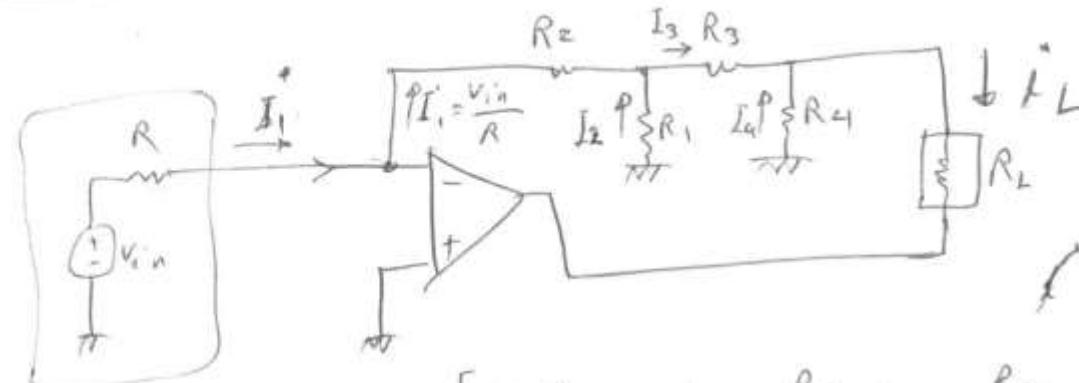
$$i_L = \frac{V_{in}}{R} + \frac{R_2 \left( \frac{V_{in}}{R} \right)}{R_1} = \frac{V_{in}}{R} \left[ \frac{R_1 + R_2}{R_1} \right] = \frac{V_{in}}{R} \left( 1 + \frac{R_2}{R_1} \right)$$



4


$$i_L = \frac{V_{in}}{R} \left[ \left( \frac{R_2}{R_4} \right) \left( 1 + \frac{R_3}{R_1} \right) + \frac{R_2}{R_1} + \frac{R_3}{R_4} + 1 \right]$$

$$I_1 = \frac{V_{in}}{R}$$

$$I_2 = \frac{I_1 R_2}{R_1} \rightarrow I_3 = I_1 + I_2 = I_1 \left( 1 + \frac{R_2}{R_1} \right)$$

$$I_4 = \frac{R_3 I_3 + R_2 I_1}{R_4} = \frac{\left( R_3 \left( 1 + \frac{R_2}{R_1} \right) + R_2 \right) I_1}{R_4}$$
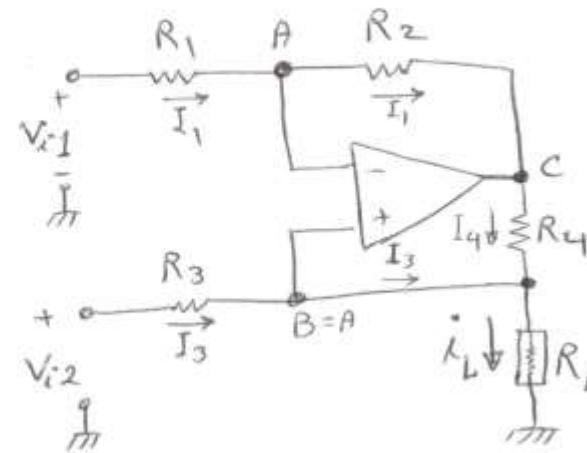
$$I_L = I_3 + I_4 = I_1 \left( \left( 1 + \frac{R_2}{R_1} \right) + \frac{R_2}{R_4} + \left( \frac{R_3 \left( 1 + \frac{R_2}{R_1} \right)}{R_4} \right) \right) = \dots$$



Howland

مدل و مرجع حمل ۱

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} \quad \text{برای:}$$

$$i_L = \frac{V_{i2} - V_{i1}}{R_3}$$

$$R_o = \frac{R_4}{\frac{R_2}{R_1} - \frac{R_4}{R_3}} = \frac{R_4}{\frac{R_2 - R_4}{R_1}} = \infty \quad \text{برای: } \omega$$

$$I_1 = \frac{V_{i1} - V_A}{R_1} = \frac{V_A - V_C}{R_2} \rightarrow V_A - V_C = \frac{R_2}{R_1} (V_{i1} - V_A)$$

$$I_3 = \frac{V_{i2} - V_A}{R_3}, \quad I_4 = \frac{V_C - V_A}{R_4}$$

$$i_L = I_3 + I_4 = \frac{V_{i2} - V_A}{R_3} + \frac{V_C - V_A}{R_4} = \frac{R_2}{R_1 R_4} (V_A - V_{i1}) + \frac{V_{i2} - V_A}{R_3} = \frac{V_A}{R_L}$$

$$\Rightarrow V_A \left[ \frac{R_2}{R_1 R_4} - \frac{1}{R_3} - \frac{1}{R_L} \right] = V_{i1} \left( \frac{R_2}{R_1 R_4} \right) - V_{i2} \left( \frac{1}{R_3} \right)$$

$$\Rightarrow V_A = \frac{V_{i2} \left( \frac{1}{R_3} \right) - V_{i1} \left( \frac{R_2}{R_1 R_4} \right)}{\frac{1}{R_3} + \frac{1}{R_L} - \frac{R_2}{R_1 R_4}} = \left[ \text{''} \right]$$

$$R > R_L$$



$$\Rightarrow V_A = \frac{V_{i2} \left( \frac{1}{R_3} \right) - V_{i1} \left( \frac{R_2}{R_1 R_4} \right)}{\frac{1}{R_3} + \frac{1}{R_L} - \frac{R_2}{R_1 R_4}} = ["]$$

$$i_L = \frac{V_A}{R_L} = \frac{1}{R_L} ["] \Rightarrow \boxed{i_L = \left( \frac{R_L}{R_3} + 1 - \frac{R_2 R_L}{R_1 R_4} \right)}$$

با اینجا می‌باشد؛ درینجا می‌باشد:  $R_L$  برای  $i_L$  چه کار کند؟

$$\frac{1}{R_3} = \frac{R_2}{R_1 R_4} \rightarrow \boxed{\frac{R_4}{R_3} = \frac{R_2}{R_1}}$$

$$i_L = V_{i2} \left( \frac{1}{R_3} \right) - V_{i1} \left( \frac{R_2}{R_1 R_4} \right) \Rightarrow \boxed{i_L = \frac{V_{i2} - V_{i1}}{R_3}}$$

---


$$\boxed{i_L = \frac{-V_{i1}}{R_3}} \Leftrightarrow \boxed{V_{i2} = 0} : \text{Howland inverting} \quad \text{کل ①}$$


$$\boxed{i_L = \frac{V_{i2}}{R_3}} \Leftrightarrow \boxed{V_{i1} = 0} : \text{Howland noninverting} \quad \text{کل ②}$$



V-I-C

محض دو-کاربره مدار و مجموع حمل

II Howland Improved.

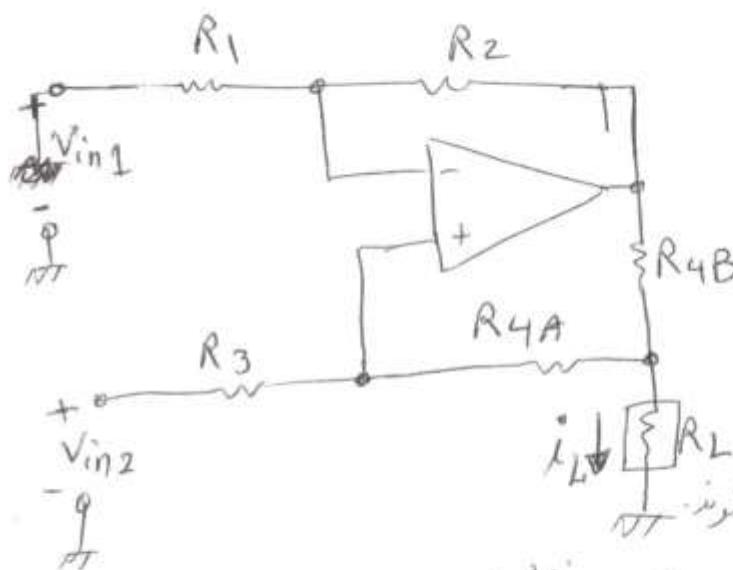

$$\frac{R_{4A} + R_{4B}}{R_3} = \frac{R_2}{R_1} \quad \text{با شرط}$$

$$i_L = (V_{in2} - V_{in1}) \left( \frac{R_2}{R_1 R_{4B}} \right)$$

بررسی انتخاب مترین  $R_4, R_3, R_2, R_1$


حد ممکن پلیوک (انتخاب مترنور - بدون منفیور)

1- حساسیت (مجموع استحال) مدار نمایاد مترنور

$V_L$  از  $V_{Com}$  ،  $V_L \leq V_d$  ممکن - ۲



مدار کالیبره کردن (۵) : (Improved V-I-C)

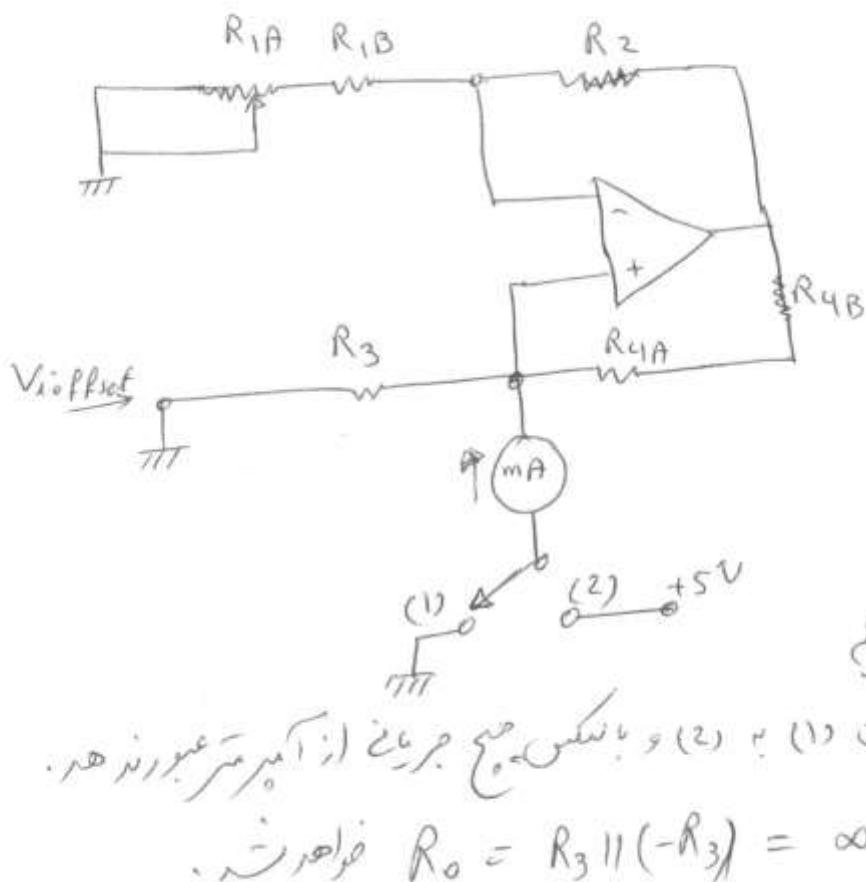

$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$

$$(R_{1A} + R_{1B} = R_1)$$

این میان خطای اتصالات و سوپریوریتی را کنترل کنید.

روش کالیبره کردن :

۱) اندر تغیر رهم با درجای

$V_i = 0$  تغیر و قیمت ملیخ (از حالت (۱) و (۲) و بانکس صحیح جریان (از آمپر متر عبور نماید).

در (۱) نت :

$$R_0 = R_3 || (-R_3) = \infty$$




۱

## محبی سوم - کاربرد مدارات مجمع محض

فصل دوازدهم: پیش‌گیردن و مقابله بازی قطعات پیسو الکترونیکی توسط IC

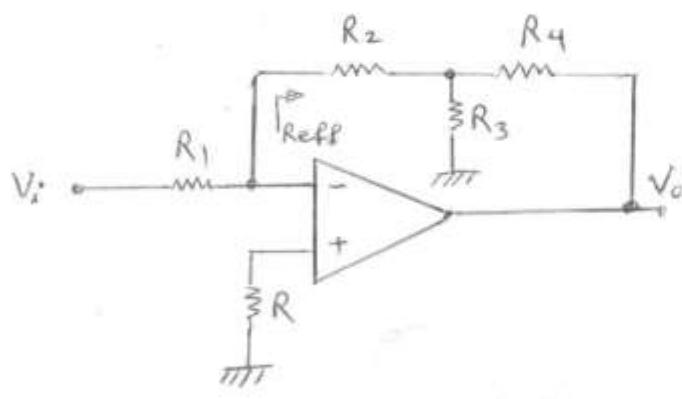۱۲-۱) افزایش مقاومت (برای دستیابی به برد بیشتر توسط مقاومتی کوچک):




\* استفاده از تبدیل T

$$Reff = R_2 + R_4 + \frac{R_2 R_4}{R_3}$$

$$V_o = -\text{Gain} \cdot V_i$$

$$\text{Gain} = \frac{Reff}{R_1}$$

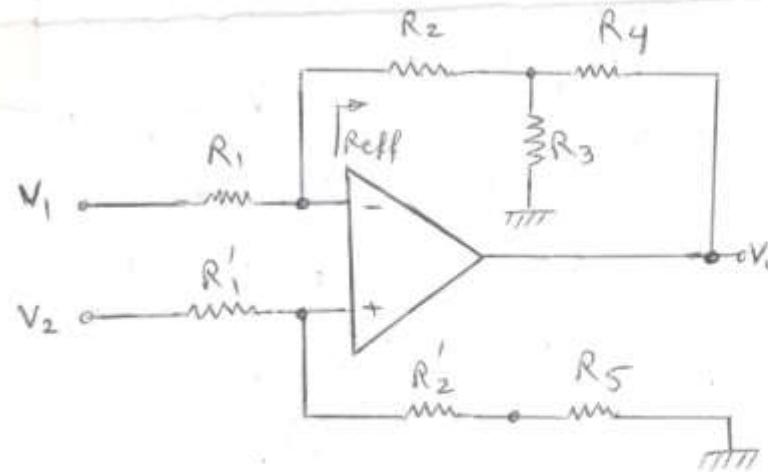


: جیویٹ نویس \*

$$\left. \begin{array}{l} R_1 = R'_1 \\ R_2 = R'_2 \\ R_5 = R_4 \parallel R_3 \end{array} \right\} \text{بامرفن}$$

$$R_{\text{eff}} = R_2 + R_4 + \frac{R_2 R_4}{R_3}$$

$$V_0 = (V_2 - V_1) \text{Gain}$$
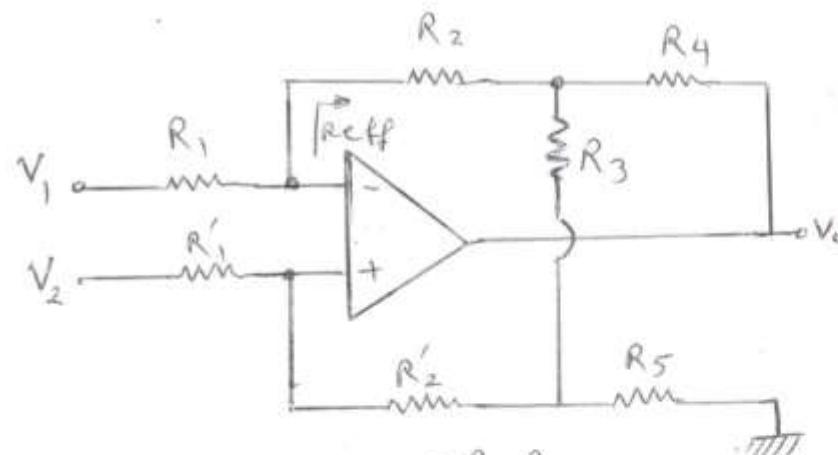
$$\text{Gain} = \frac{R_{\text{eff}}}{R_1}$$



: جیویٹ نویس / جیویٹ نویس \*

$$\left. \begin{array}{l} R_1 = R'_1 \\ R_2 = R'_2 \\ R_5 = R_4 \end{array} \right\} \text{بامرفن}$$


$$R_{\text{eff}} = R_2 + R_4 + \frac{2 R_2 R_4}{R_3}$$

$$V_0 = (V_2 - V_1) \text{Gain}$$

$$\text{Gain} = \frac{R_{\text{eff}}}{R_1}$$
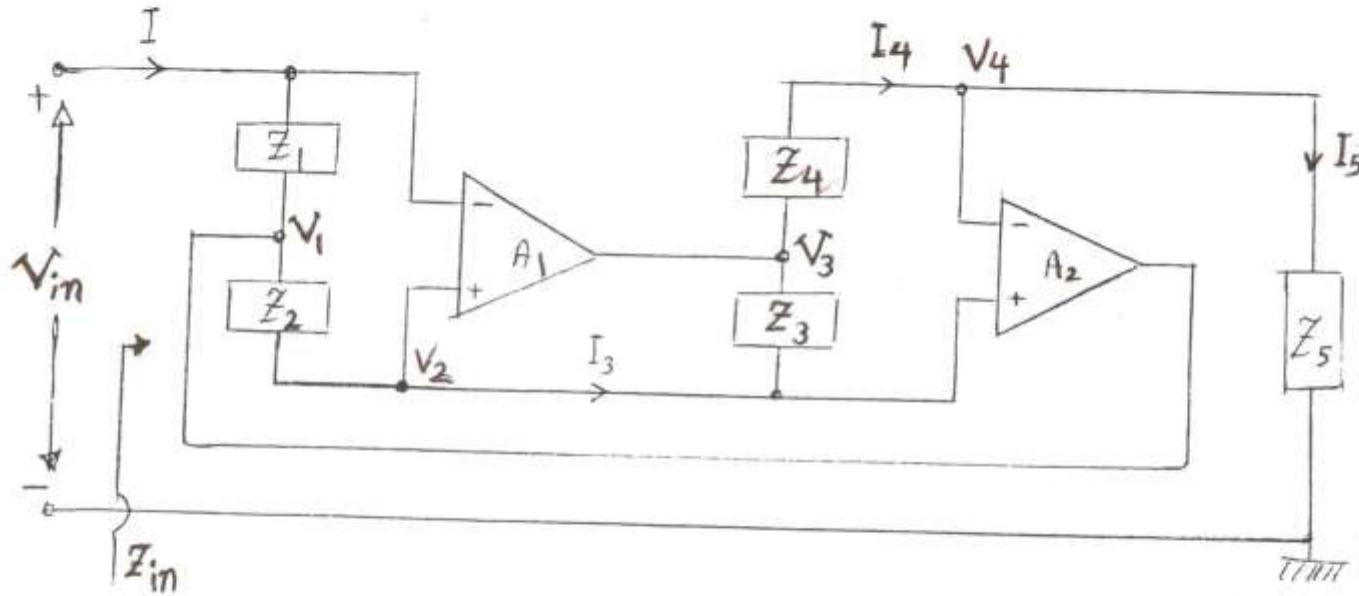
# مجسٹر سریم - کاروڈ مدارات پسختہ

(General Impedance Converter) : (GIC) میل امپیانس (Milliampere)



$$V_{in} = V_2 = V_4, \quad I_4 = I_5 = \frac{V_4}{Z_5} \quad : \text{پہلے OP-Amp کا ترمومتریک مکانیزم}$$

$$V_3 = V_4 + I_4 Z_4, \quad I_3 = \frac{V_2 - V_3}{Z_3} = - V_{in} \frac{Z_4}{Z_3 Z_5}$$

$$I = \frac{V_{in} - V_1}{Z_1} = V_{in} \frac{Z_4 Z_2}{Z_1 Z_3 Z_5} \Rightarrow Z_{in} = \frac{V_{in}}{I} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$



$$I = \frac{V_{in} - V_1}{Z_1} = V_{in} \frac{Z_4 Z_2}{Z_1 Z_3 Z_5} \Rightarrow Z_{in} = \frac{V_{in}}{I} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

: حال اگر در این راسته  $Z_4$  و  $Z_2$  را خازن بینه (و بقیه مقادیر) داریم  $\Rightarrow$  (I)

$$Z_{in} = \frac{R_1 R_3 R_5}{\frac{1}{j\omega C_2} \cdot R_4} = j\omega C_2 \frac{R_1 R_3 R_5}{R_4}$$

عمل مدار مثل مک سلف عمل نمایند

$$L = C_2 \frac{R_1 R_3 R_5}{R_4}$$

: در این راسته  $\Rightarrow$

$$C_{in} = C_1 \frac{R_2 R_4}{R_3 R_5} \quad \text{حال اگر } Z_1, Z_3 \text{ و } Z_5 \text{ خازن بینه در این راسته : (II)}$$

مثال عددی: ۱) مدار از توپ درسته است:

$$R_1 = R_3 = R_5 = R_4 = 10\text{K}, C_2 = 1\text{nF}$$

$$\Rightarrow L = 0.1\text{H}$$

(ترجمه: نک این مدار را با مقادیر مذکور تبلیغ نمایند)


$$Z_{in} = 11.6 + j\omega 0.16$$

$$\Leftrightarrow \begin{cases} Z_1 = Z_3 = Z_5 = 2\text{K}\Omega \\ Z_2 = 1\text{K}\Omega \end{cases}$$

مثال عددی ۲) فرزن بینه:



# Logarithmic Amplifier

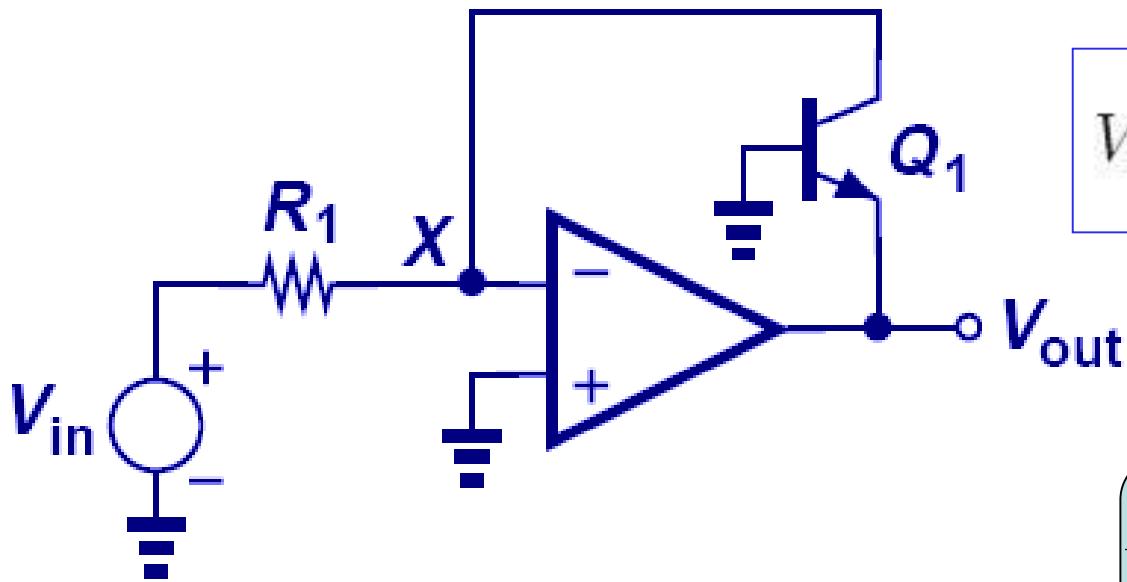

$$V_{BE} = V_T \ln \frac{V_{in}/R_1}{I_S}.$$

$$V_{out} = -V_T \ln \frac{V_{in}}{R_1 I_S}$$


- By inserting a bipolar transistor in the loop, an amplifier with logarithmic characteristic can be constructed.
- This is because the current to voltage conversion of a bipolar transistor is a natural logarithm.



# Square-Root Amplifier

$$V^- \approx V^+$$

$$I_{in1} = I_{in2} \approx 0$$



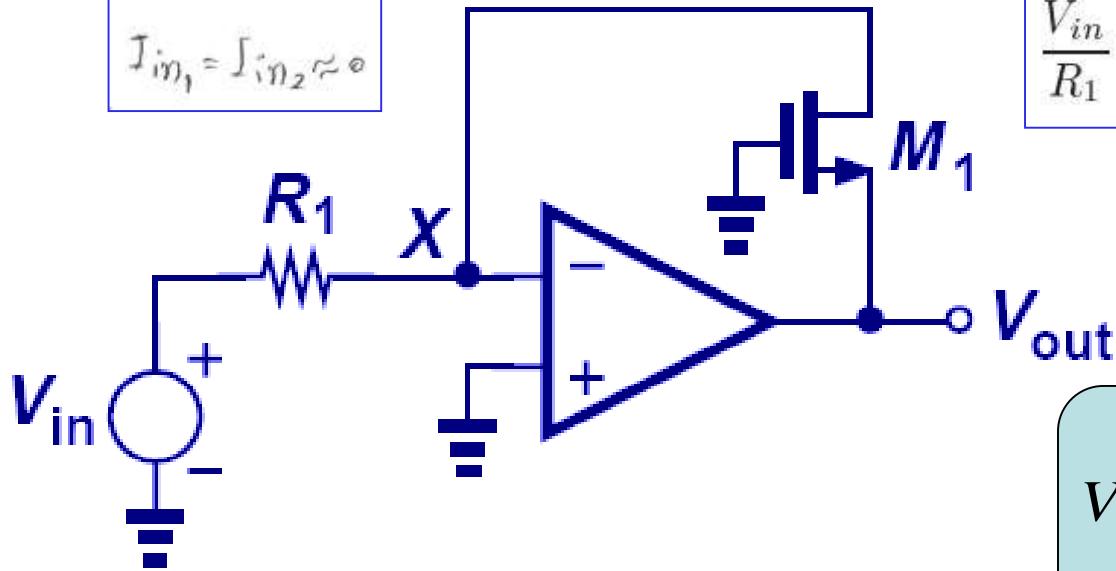


$$\frac{V_{in}}{R_1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2.$$

$$V_{out} = - \sqrt{\frac{2V_{in}}{\mu_n C_{ox} \frac{W}{L} R_1}} - V_{TH}$$


- By replacing the bipolar transistor with a MOSFET, an amplifier with a square-root characteristic can be built.
- This is because the current to voltage conversion of a MOSFET is square-root.

# Op Amp Nonidealities: DC Offsets

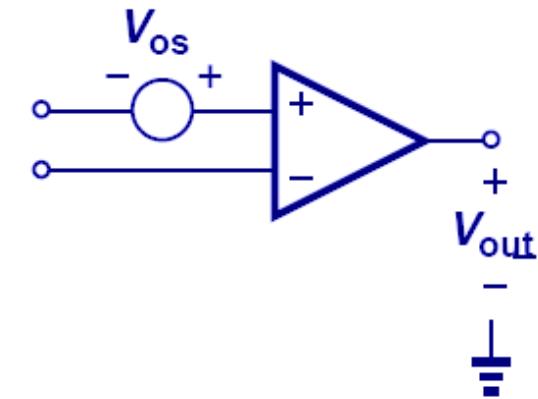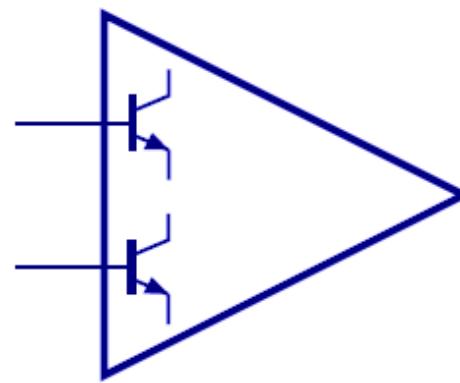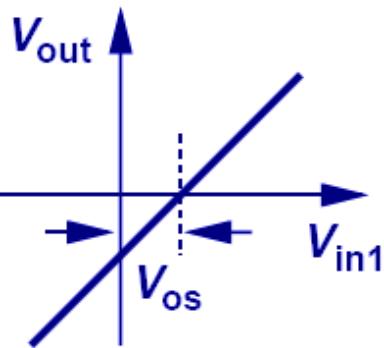

- Offsets in an op amp that arise from input stage mismatch cause the input-output characteristic to shift in either the positive or negative direction (the plot displays positive direction).

## Effects of DC Offsets

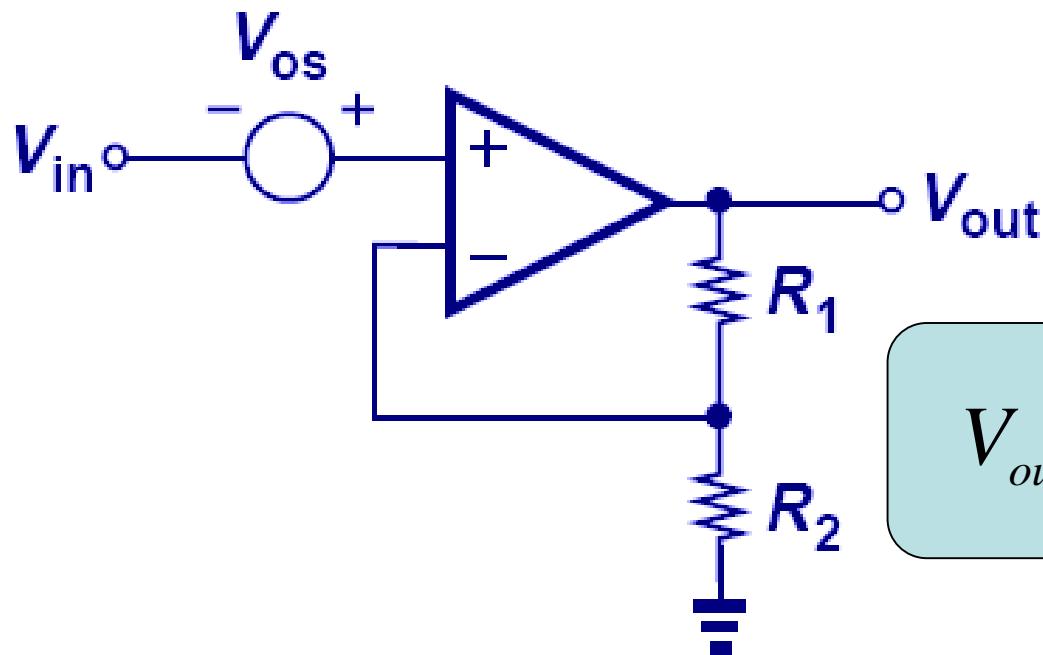


$$V_{out} = \left(1 + \frac{R_1}{R_2}\right)(V_{in} + V_{os})$$

- As it can be seen, the op amp amplifies the input as well as the offset, thus creating errors.




## Saturation Due to DC Offsets

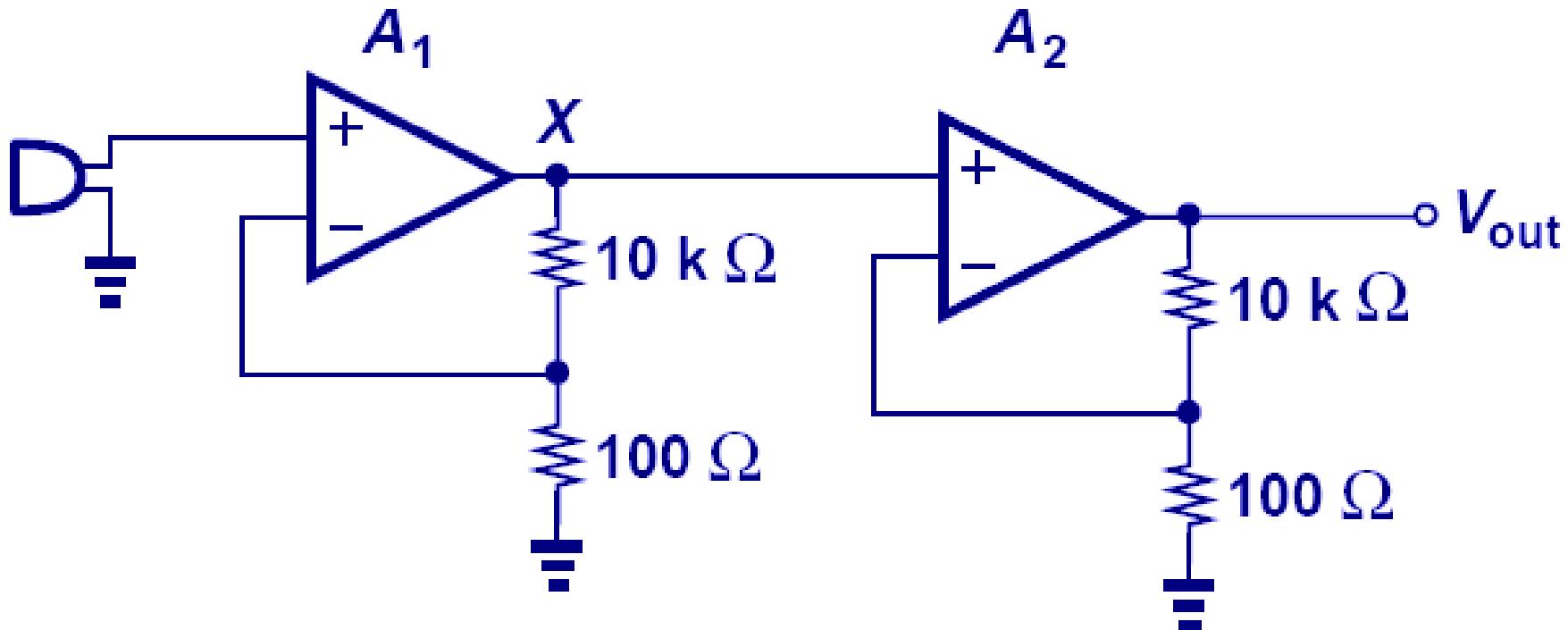


- Since the offset will be amplified just like the input signal, output of the first stage may drive the second stage into saturation.




# Offset in Integrator

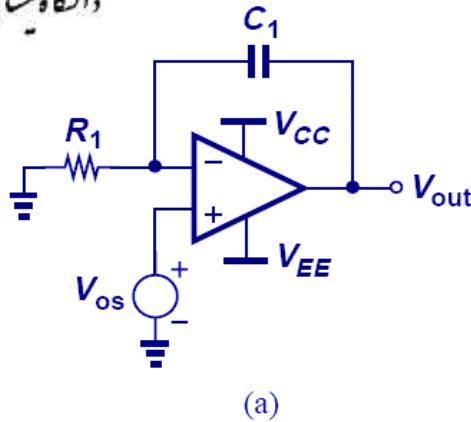


(a)

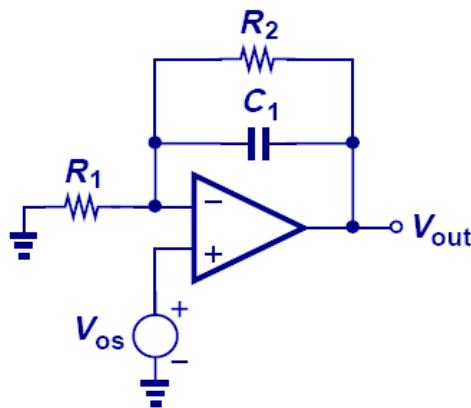

(c)

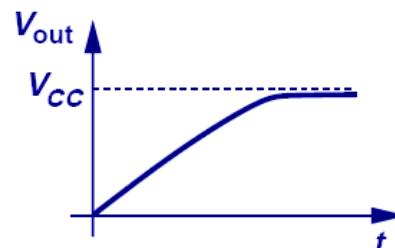

(b)

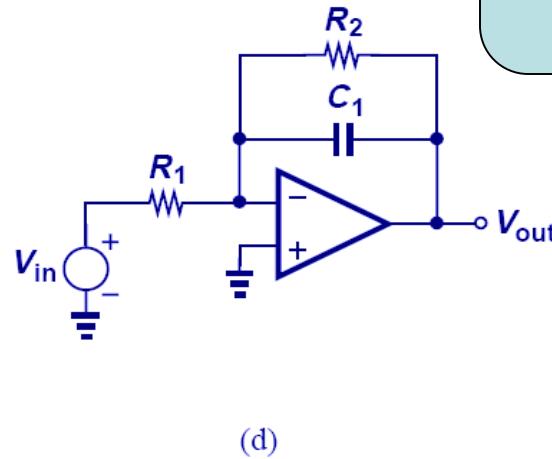


(d)

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \frac{1}{R_2 C_1 s + 1}$$

- A resistor can be placed in parallel with the capacitor to “absorb” the offset. However, this means the closed-loop transfer function no longer has a pole at origin.


# Input Bias Current

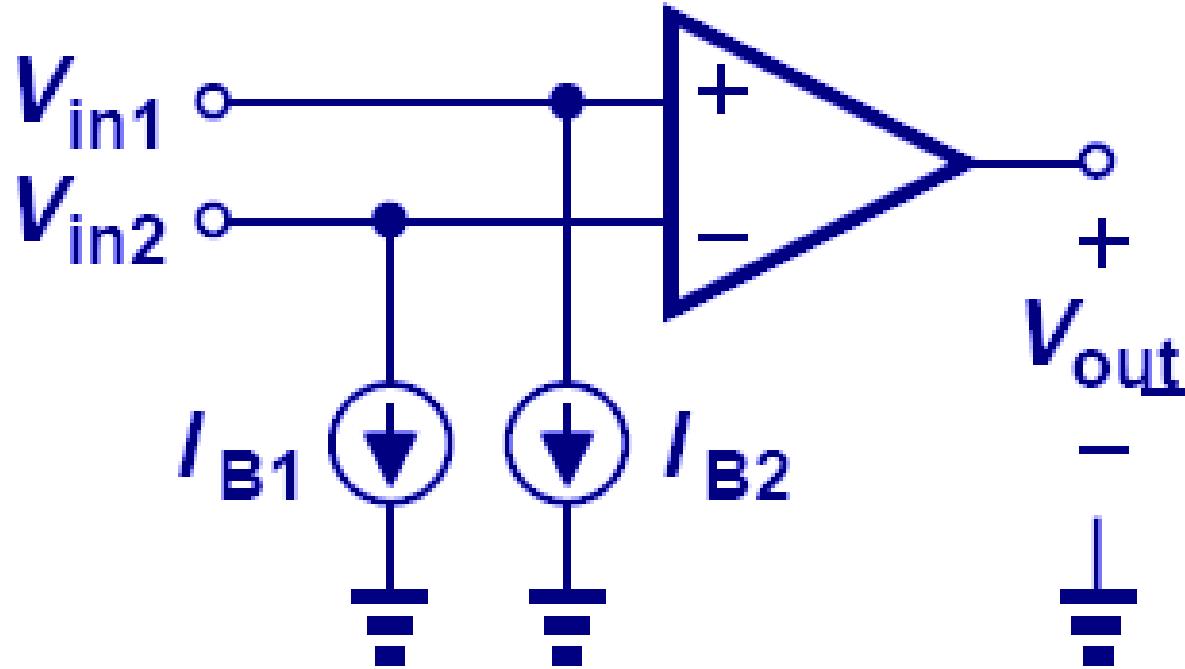


- The effect of bipolar base currents can be modeled as current sources tied from the input to ground.



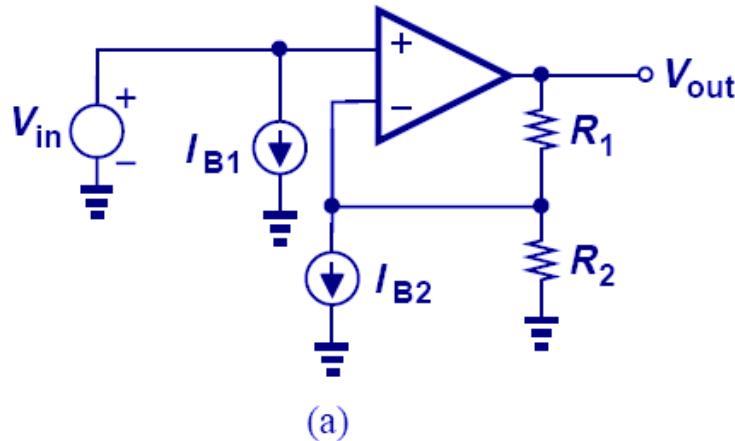
## Effects of Input Bias Current on Noninverting Amplifier



(a)

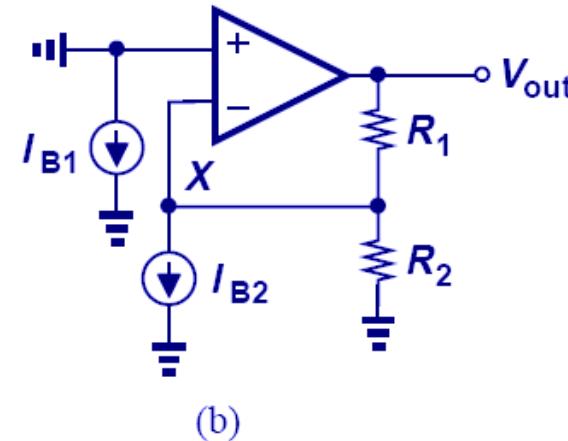

(b)

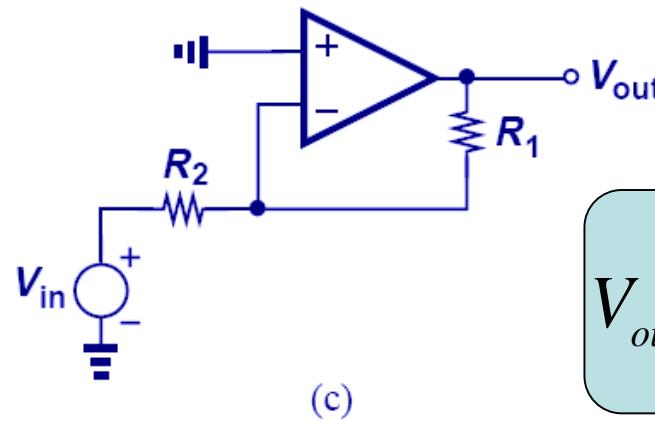


(c)

$$V_{out} = -R_2 I_{B2} \left( -\frac{R_1}{R_2} \right) = R_1 I_{B2}$$

► It turns out that  $I_{B1}$  has no effect on the output and  $I_{B2}$  affects the output by producing a voltage drop across  $R_1$ .


# Input Bias Current Cancellation

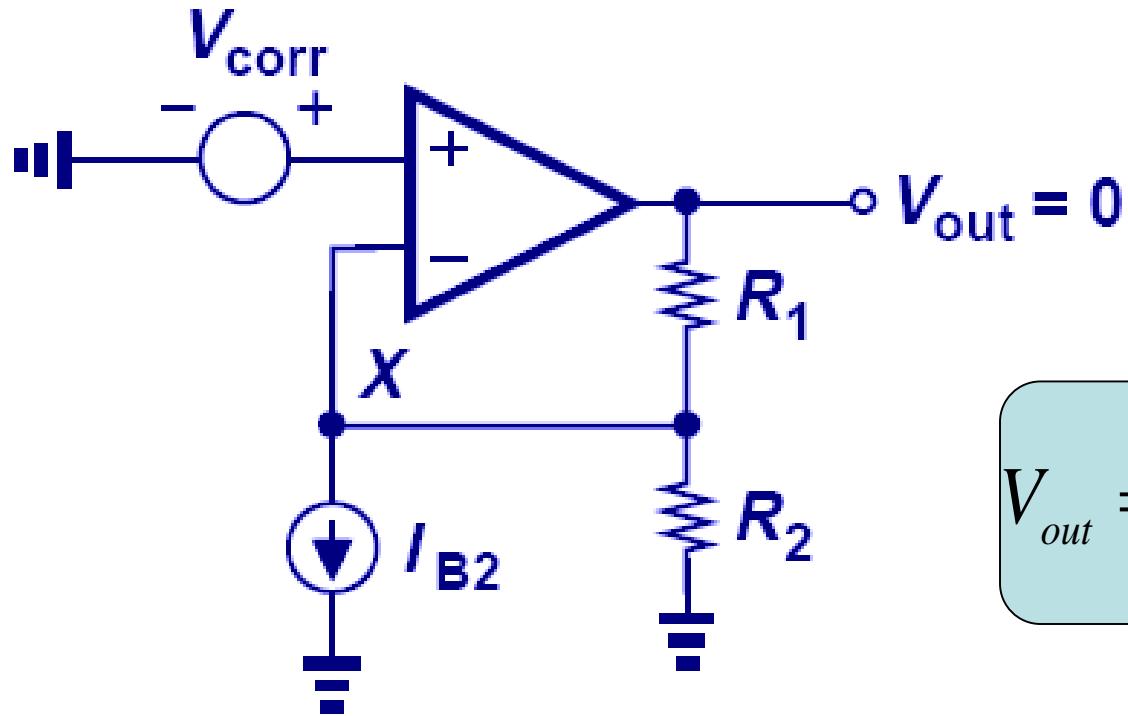

$$V_{out} = V_{corr} \left( 1 + \frac{R_1}{R_2} \right) + I_{B2} R_1$$

- We can cancel the effect of input bias current by inserting a correction voltage in series with the positive terminal.
- In order to produce a zero output,  $V_{corr} = -I_{B2}(R_1 || R_2)$ .



## Correction for $\beta$ Variation

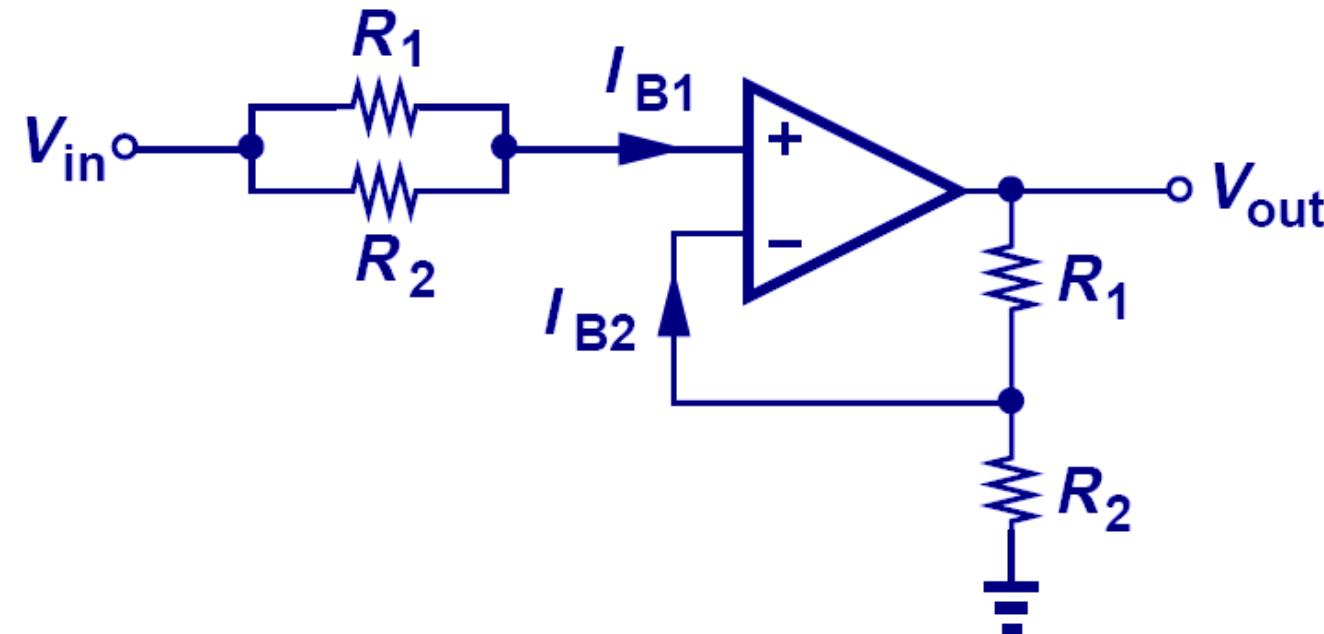

- Since the correction voltage is dependent upon  $\beta$ , and  $\beta$  varies with process, we insert a parallel resistor combination in series with the positive input. As long as  $I_{B1} = I_{B2}$ , the correction voltage can track the  $\beta$  variation.



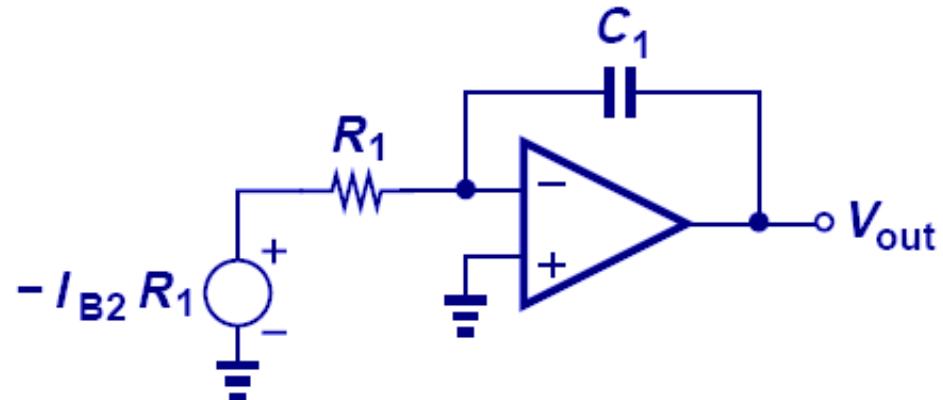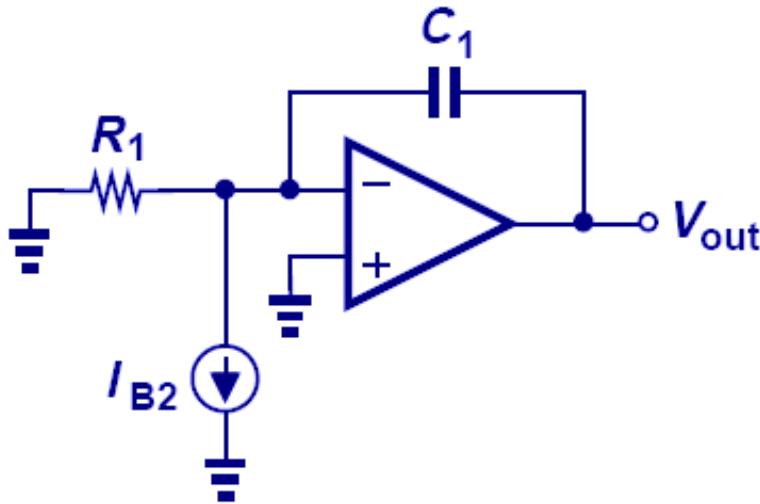
# Effects of Input Bias Currents on Integrator



$$V_{out} = -\frac{1}{R_1 C_1} \int (-I_{B2} R_1) dt$$


- **Input bias current will be integrated by the integrator and eventually saturate the amplifier.**
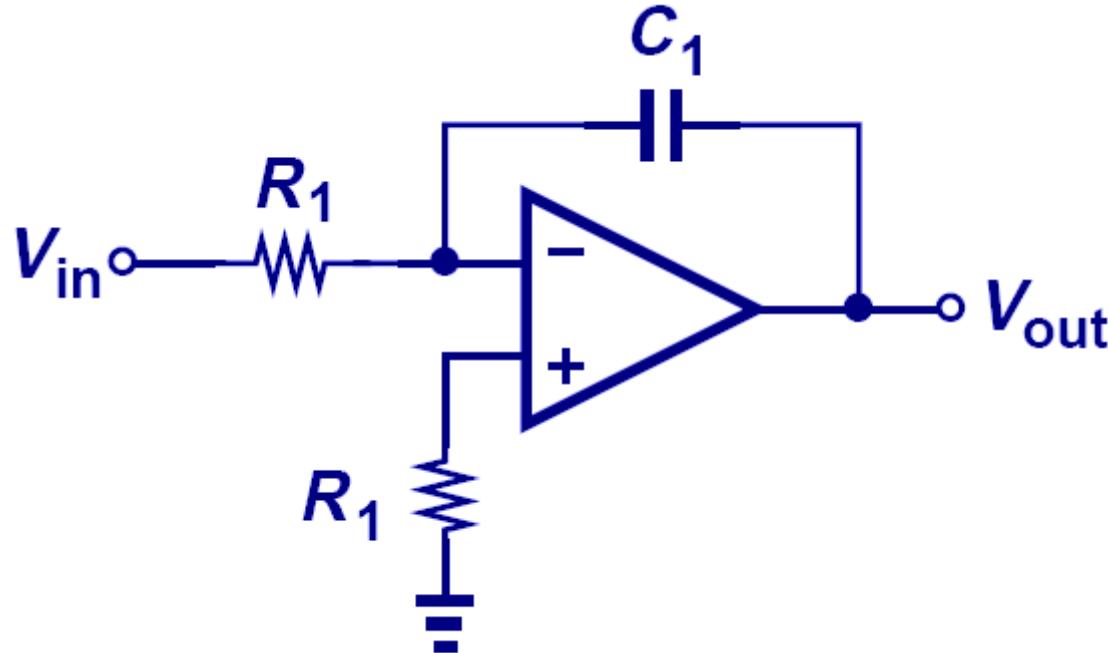
# Integrator's Input Bias Current Cancellation



- By placing a resistor in series with the positive input, integrator input bias current can be cancelled.
- However, the output still saturates due to other effects such as input mismatch, etc.


## Speed Limitation

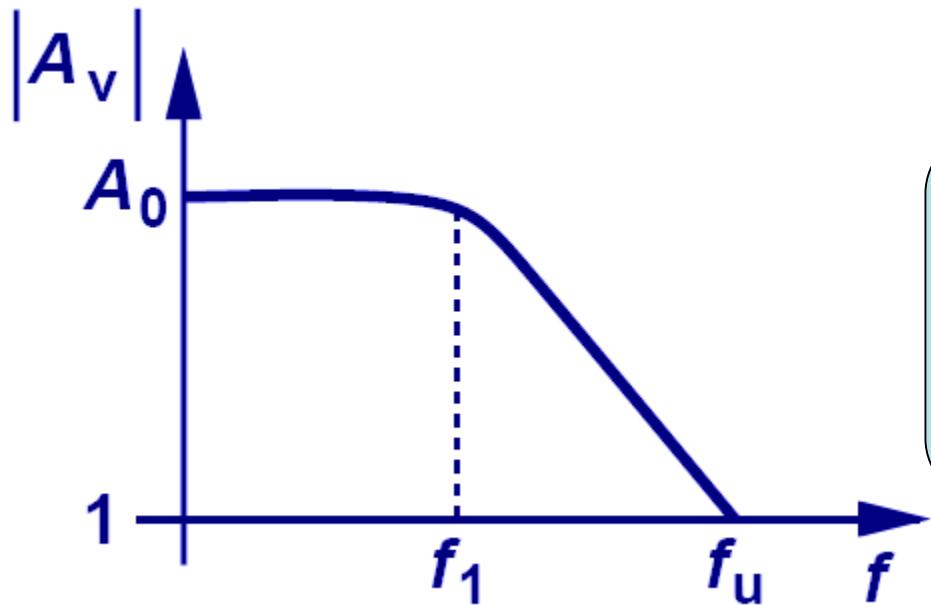

$$\frac{V_{out}}{V_{in1} - V_{in2}}(s) = \frac{A_0}{1 + \frac{s}{\omega_1}}$$

- Due to internal capacitances, the gain of op amps begins to roll off.




## Bandwidth and Gain Tradeoff

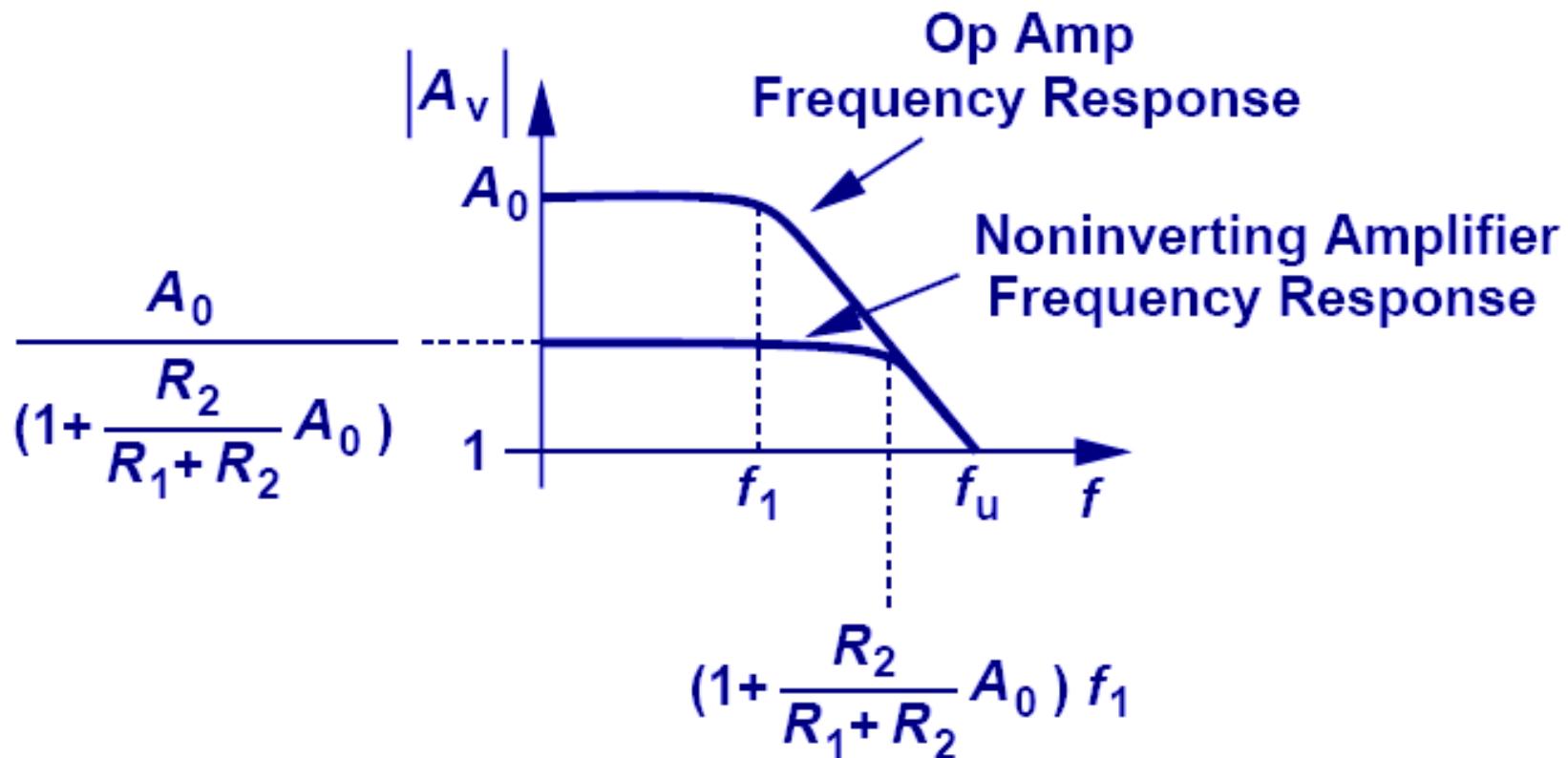

- Having a loop around the op amp (inverting, noninverting, etc) helps to increase its bandwidth. However, it also decreases the low frequency gain.




# Slew Rate of Op Amp

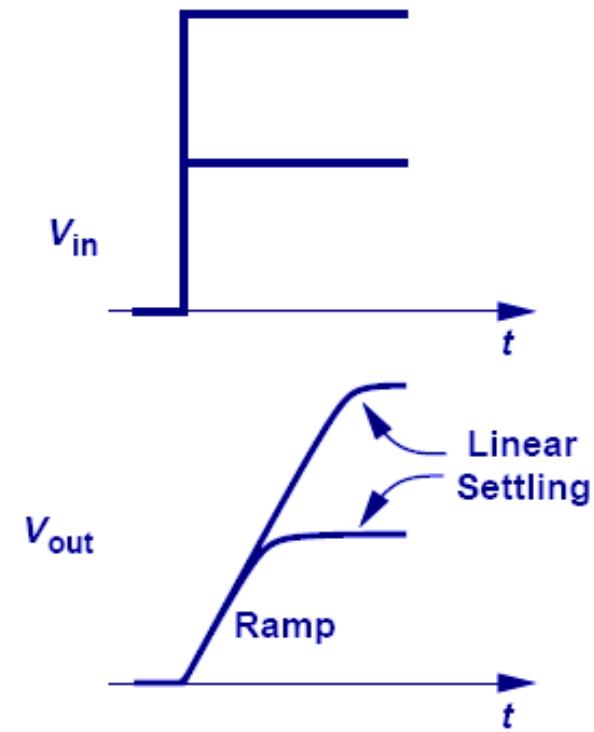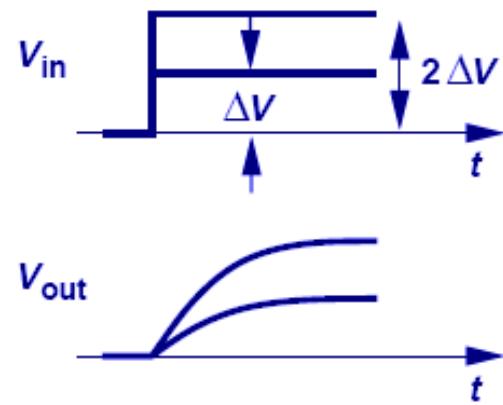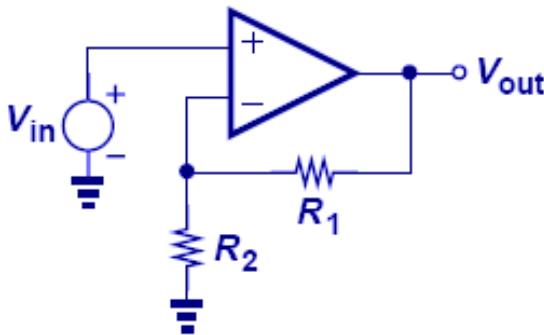

- In the linear region, when the input doubles, the output and the output slope also double. However, when the input is large, the op amp slews so the output slope is fixed by a constant current source charging a capacitor.
- This further limits the speed of the op amp.
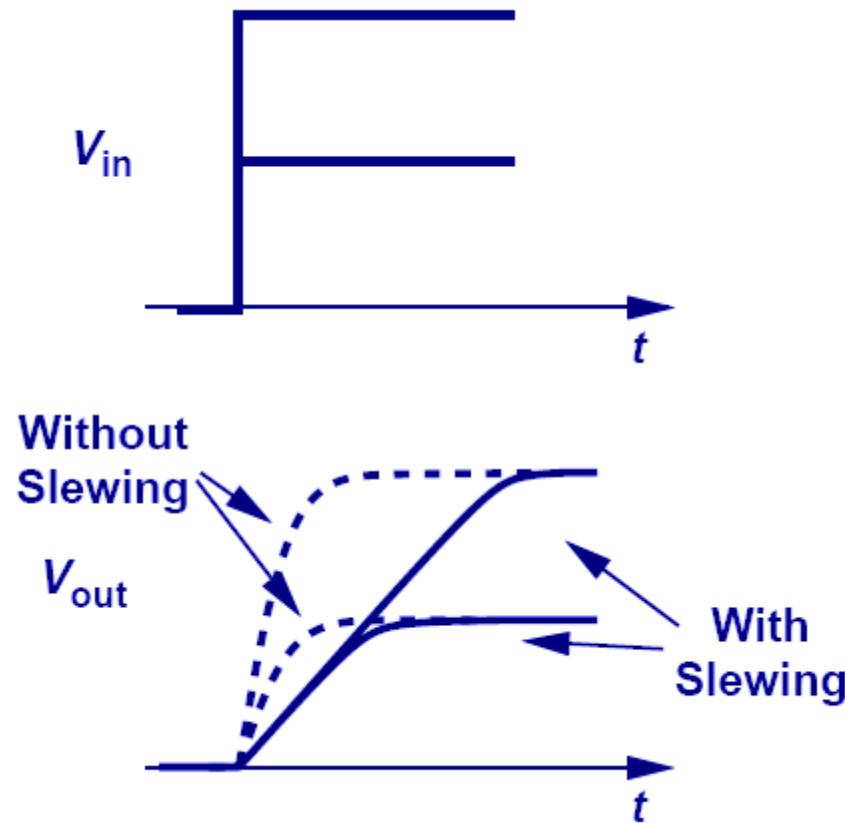
## Comparison of Settling with and without Slew Rate




- As it can be seen, the settling speed is faster without slew rate (as determined by the closed-loop time constant).




# Slew Rate Limit on Sinusoidal Signals


دانشگاه تهران  
دانشکده فنی

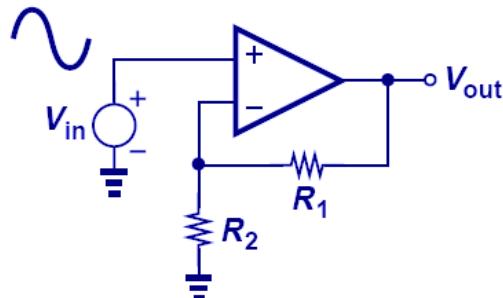

(a)

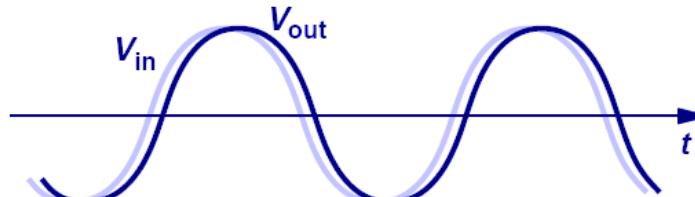

(b)

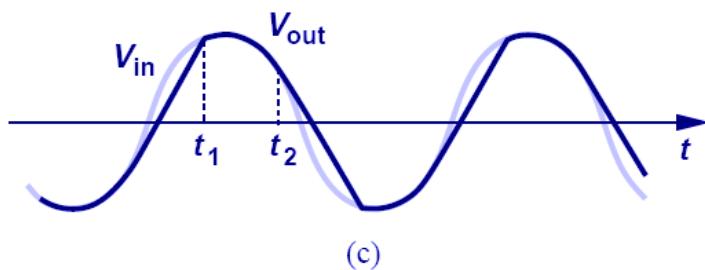



(c)

$$\frac{dV_{out}}{dt} = V_0 \left( 1 + \frac{R_1}{R_2} \right) \omega \cos \omega t$$

- As long as the output slope is less than the slew rate, the op amp can avoid slewing.
- However, as operating frequency and/or amplitude is increased, the slew rate becomes insufficient and the output becomes distorted.



# Maximum Op Amp Swing

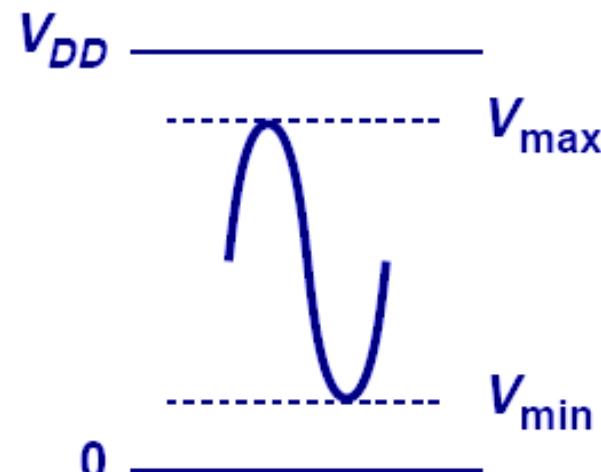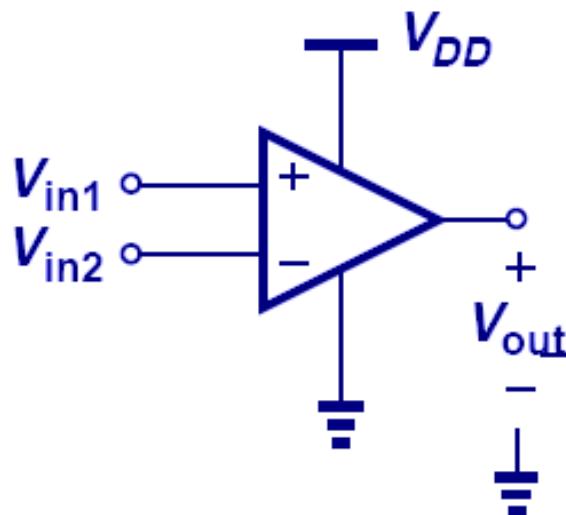



$$V_{out} = \frac{V_{max} - V_{min}}{2} \sin \omega t + \frac{V_{max} + V_{min}}{2} \quad \omega_{FP} = \frac{SR}{\frac{V_{max} - V_{min}}{2}}$$

- To determine the maximum frequency before op amp slews, first determine the maximum swing the op amp can have and divide the slew rate by it.



# Nonzero Output Resistance

دانشگاه تهران  
دانشکده فنی و مهندسی

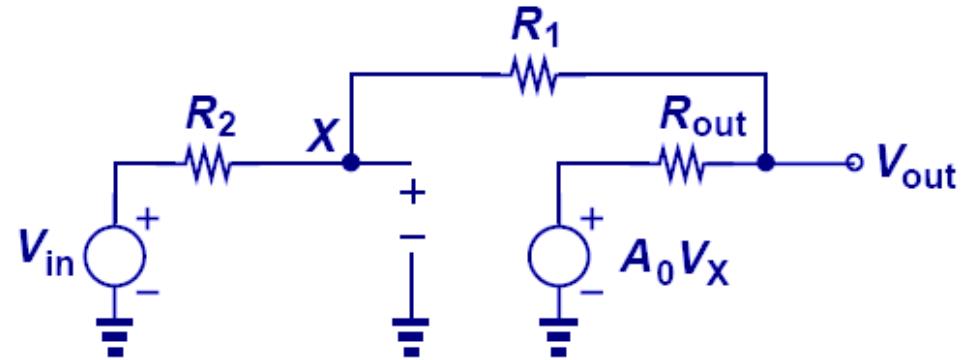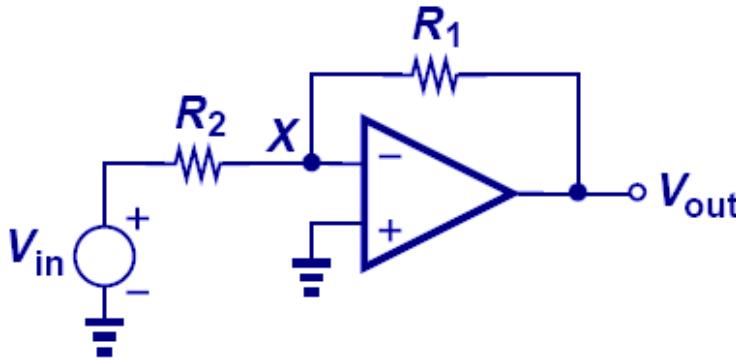

$$\frac{V_{out}}{V_{in}} = -\frac{R_1}{R_2} \frac{A_0 - \frac{R_{out}}{R_1}}{1 + \frac{R_{out}}{R_2} + A_0 + \frac{R_1}{R_2}}$$

- In practical op amps, the output resistance is not zero.
- It can be seen from the closed loop gain that the nonzero output resistance increases the gain error.



## Design Examples

- Many design problems are presented at the end of the chapter to study the effects of finite loop gain, restrictions on peak to peak swing to avoid slewing, and how to design for a certain gain error.

